



VIGNANA BHARATHI
Institute of Technology



NAAC
NATIONAL ASSESSMENT AND
ACCREDITATION COUNCIL

Counselling
Code
VBIT

VLSI

UNIT - V

Programmable Logic Devices

P.VIDYA SAGAR (ASSOCIATE PROFESSOR)



Department of Electronics and Communication Engineering, VBIT


CONTENTS

SEMICONDUCTOR INTEGRATED CIRCUIT DESIGN: PLAs, FPGAs, CPLDs, Standard Cells, Programmable Array Logic, Design Approach, Parameters influencing low power design.

CMOS TESTING: CMOS Testing, Need for testing, Test Principles, Design Strategies for test, Chip level Test Techniques.

Programmable Logic Devices (PLD)

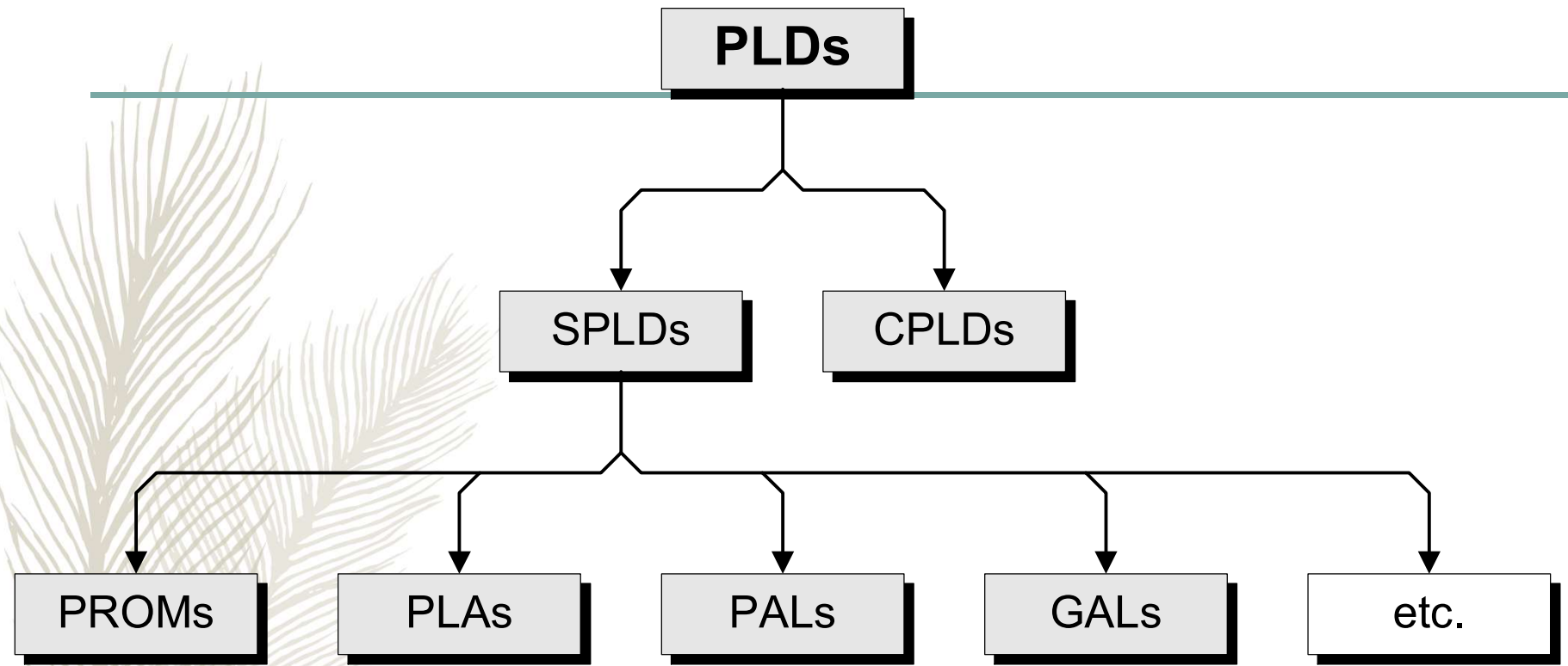
- *General purpose chip for implementing circuits*
- *Can be customized using programmable switches*
 - **Main types of PLDs**
 - *PLA*
 - *PAL*
 - *ROM*
 - *CPLD*
 - *FPGA*
- **Custom chips: standard cells, sea of gates**



PLD

- The purpose of a PLD device is to permit elaborate digital logic designs to be implemented by the user in a single device.
- Can be erased electrically and reprogrammed with a new design, making them very well suited for academic and prototyping
- Types of Programmable Logic Devices
- SPLDs (Simple Programmable Logic Devices)
 - ROM (Read-Only Memory)
 - PLA (Programmable Logic Array)
 - PAL (Programmable Array Logic)
 - GAL (Generic Array Logic)
- CPLD (Complex Programmable Logic Device)
- FPGA (Field-Programmable Gate Array)

General structure of PLDs.

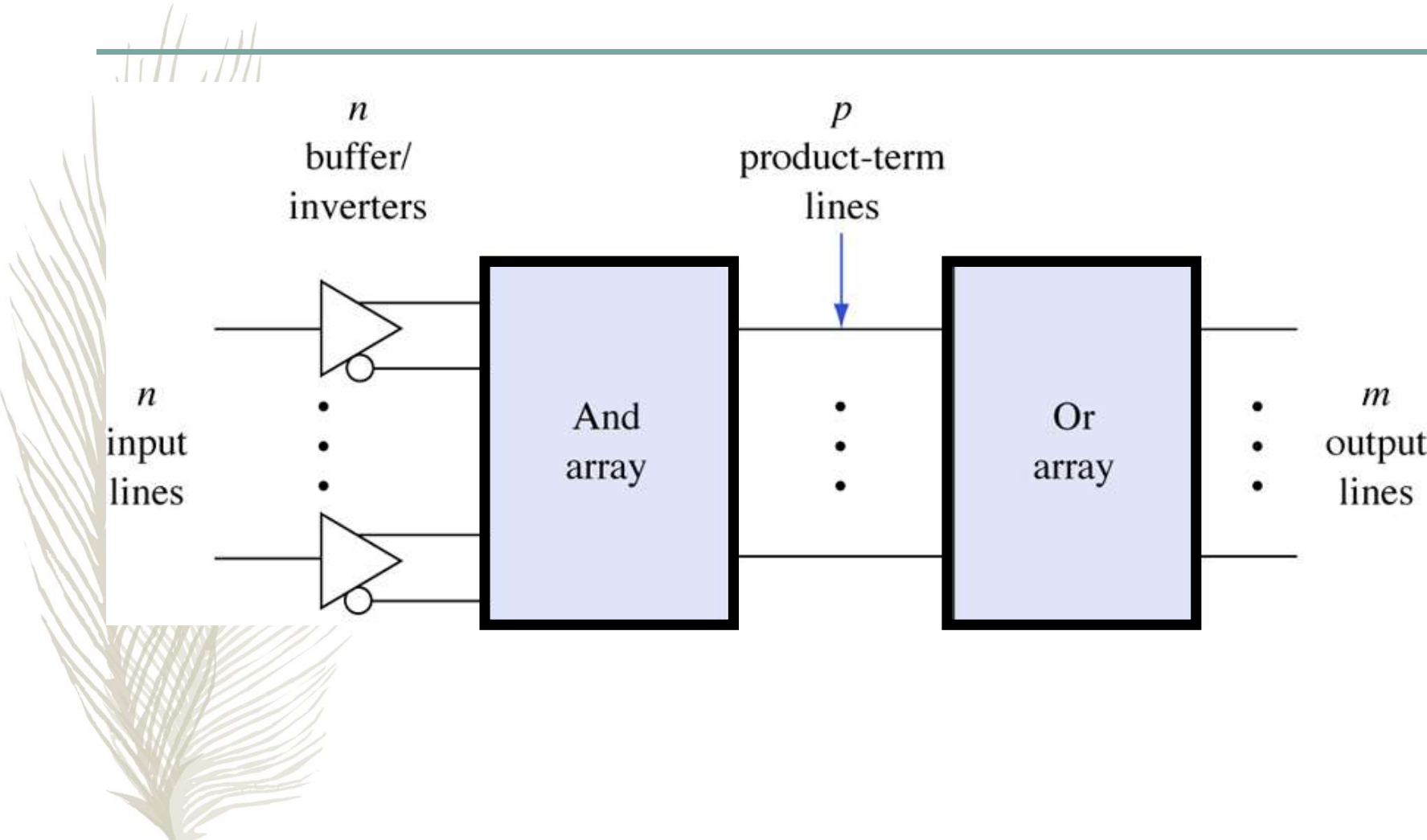


PLD

- The differences between the first three categories are these:
 - In a ROM, the input connection matrix is hardwired. The user can modify the output connection matrix.
 - In a PAL/GAL the output connection matrix is hardwired. The user can modify the input connection matrix.
 - In a PLA the user can modify both the input connection matrix and the output connection matrix.

Device	AND-array	OR-array
PROM	Fixed	Programmable
PLA	Programmable	Programmable
PAL	Programmable	Fixed
GAL	Programmable	Fixed

Programming by blowing fuses.

 

(a)


(a) Before programming.




(b)

(b) After programming.

OR - PLD Notation

 


OR gate before programming

 


OR gate after programming








AND - PLD Notation

 

AND gate before programming

 


AND gate after programming

       

ROM Internal Logic


- The decoder stage produces ALL possible minterms
- 32 Words of 8 bits each
- 5 input lines (address)
- Each OR gate has a 32 input
- A contact can be made using fuse/anti-fuse

Internal Logic of a 32x8 ROM

 

Programming a ROM

Inputs					Outputs							
I4	I3	I2	I1	I0	A7	A6	A5	A4	A3	A2	A1	A0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
.
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

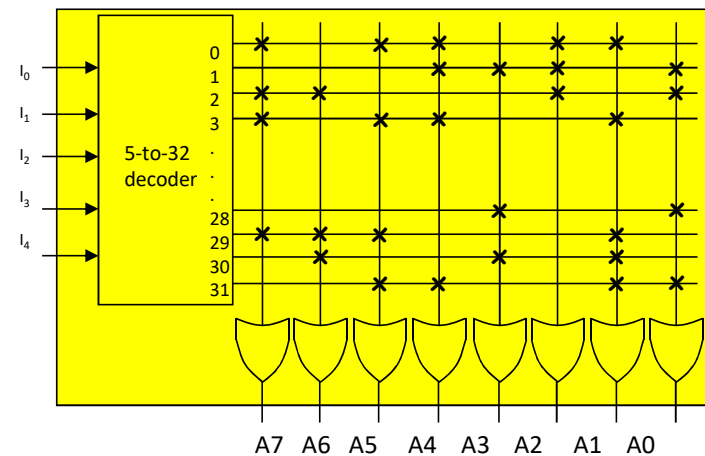

- Every ONE in truth table specifies a closed circuit
- Every ZERO in truth table specifies an OPEN circuit
- Example: At address 00011 → The word 10110010 is stored

Example 1

- **Example:** Design a combinational circuit using ROM. The circuit accepts a 3-bit number and generates an output binary number equal to the square of the number.
- **Solution:** Derive truth table:


Inputs			Outputs						
A2	A1	A0	B5	B4	B3	B2	B1	B0	SQ
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

Example 1 (cont.)

Inputs			Outputs				
A2	A1	A0	B5	B4	B3	B2	SQ
0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	1
0	1	0	0	0	0	1	4
0	1	1	0	0	1	0	9
1	0	0	0	1	0	0	16
1	0	1	0	1	1	0	25
1	1	0	1	0	0	1	36
1	1	1	1	1	0	0	49

ROM truth table – specifies the required connections

- B1 is ALWAYS 0 → no need to generate it using the ROM
- B0 is equal to A0 → no need to generate it using the ROM
- Therefore: The minimum size of ROM needed is $2^3 \times 4$ or 8×4

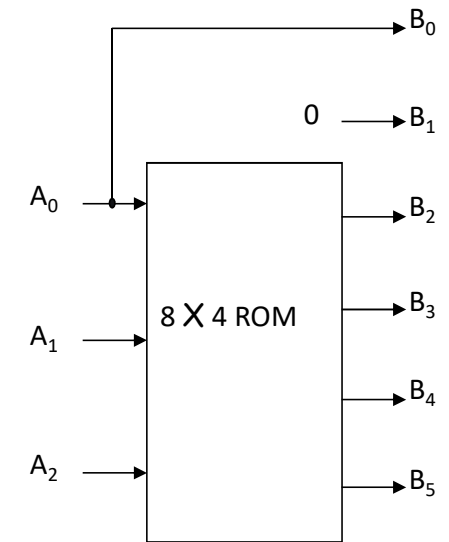


Example 2

- **Problem:** Tabulate the truth for an 8 X 4 ROM that implements the following four Boolean functions:

- $A(X,Y,Z) = \Sigma m(3,6,7)$; $B(X,Y,Z) = \Sigma m(0,1,4,5,6)$


- $C(X,Y,Z) = \Sigma m(2,3,4)$; $D(X,Y,Z) = \Sigma m(2,3,4,7)$

- **Solution:**

 

Inputs			Outputs			
X	Y	Z	A	B	C	D
0	0	0	0	1	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	1	1
1	0	1	0	1	0	0
1	1	0	1	1	0	0
1	1	1	1	0	0	1

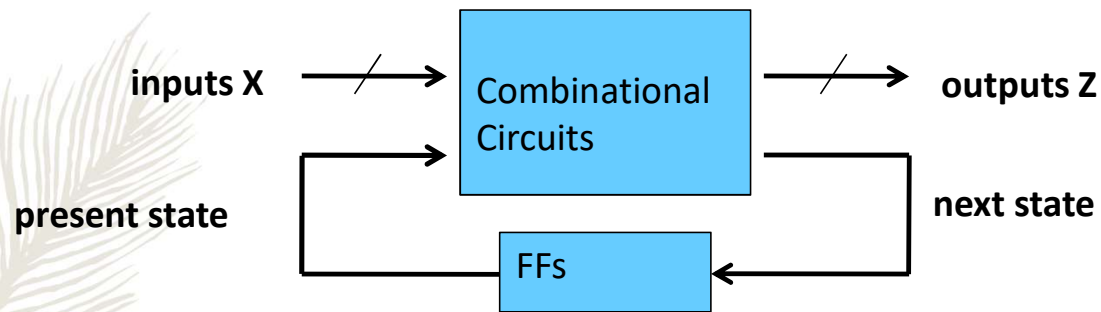Sequential Circuit Implementation with ROM



- sequential circuit = combinational circuit + memory
- Combinational part can be built with a ROM as shown previously
 - Number of address lines = No. of FF + No. of inputs
 - Number of outputs = No. of FF + No. of outputs


Example

- **Example:** Design a sequential circuit whose state table is given, using a ROM and a register.

State Table

Present State		Input	Next State		Output
Q_2	Q_1	X	Q_2^+	Q_1^+	Y
0	0	0	0	0	0
0	0	1	0	1	0
1	0	0	0	1	0
1	0	1	0	0	1
0	1	0	1	0	0
0	1	1	0	1	0
1	1	0	1	1	0
1	1	1	0	0	1

 We need a 8x3 ROM (why?)
3 address lines and 3 data lines




Exercise: Compare design with ROMs with the traditional design procedure.

Gate Level Version of PLA

$$f_1 = x_1x_2 + x_1x_3' + x_1'x_2'x_3$$

$$f_2 = x_1x_2 + x_1'x_2'x_3 + x_1x_3$$

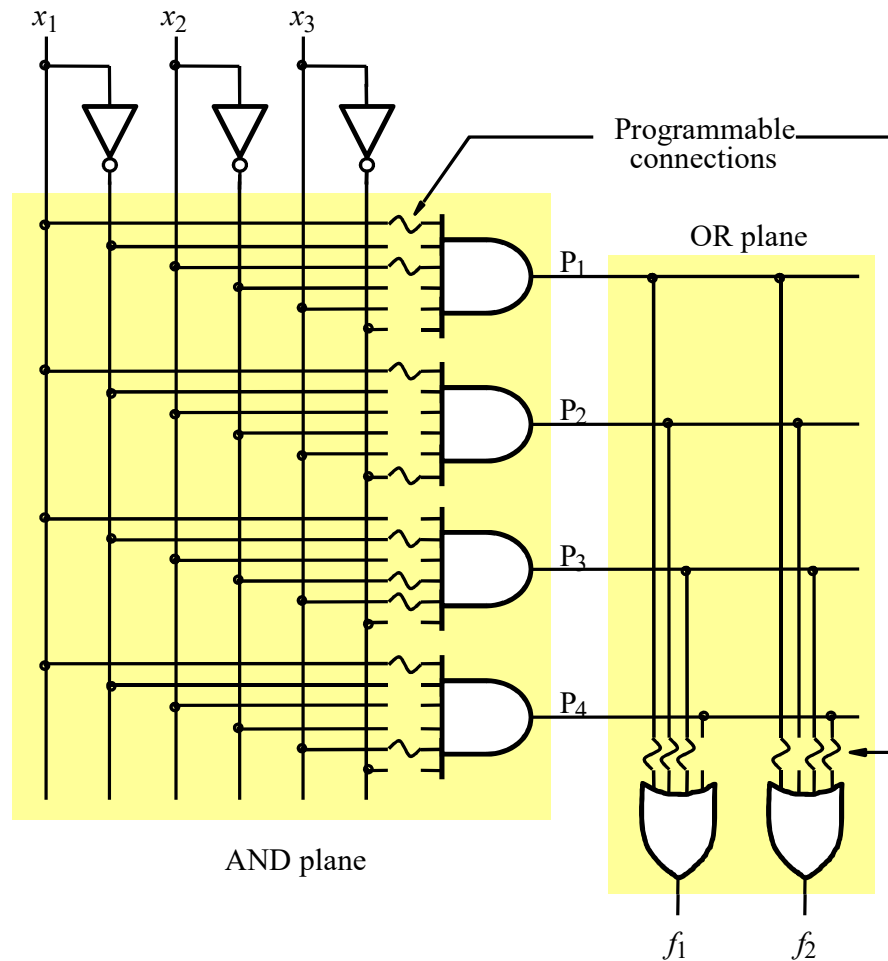


AND plane

f_1 f_2

$$f_1 = x_1x_2 + x_1x_3' + x_1'x_2'x_3$$

$$f_2 = x_1x_2 + x_1'x_2'x_3 + x_1x_3$$

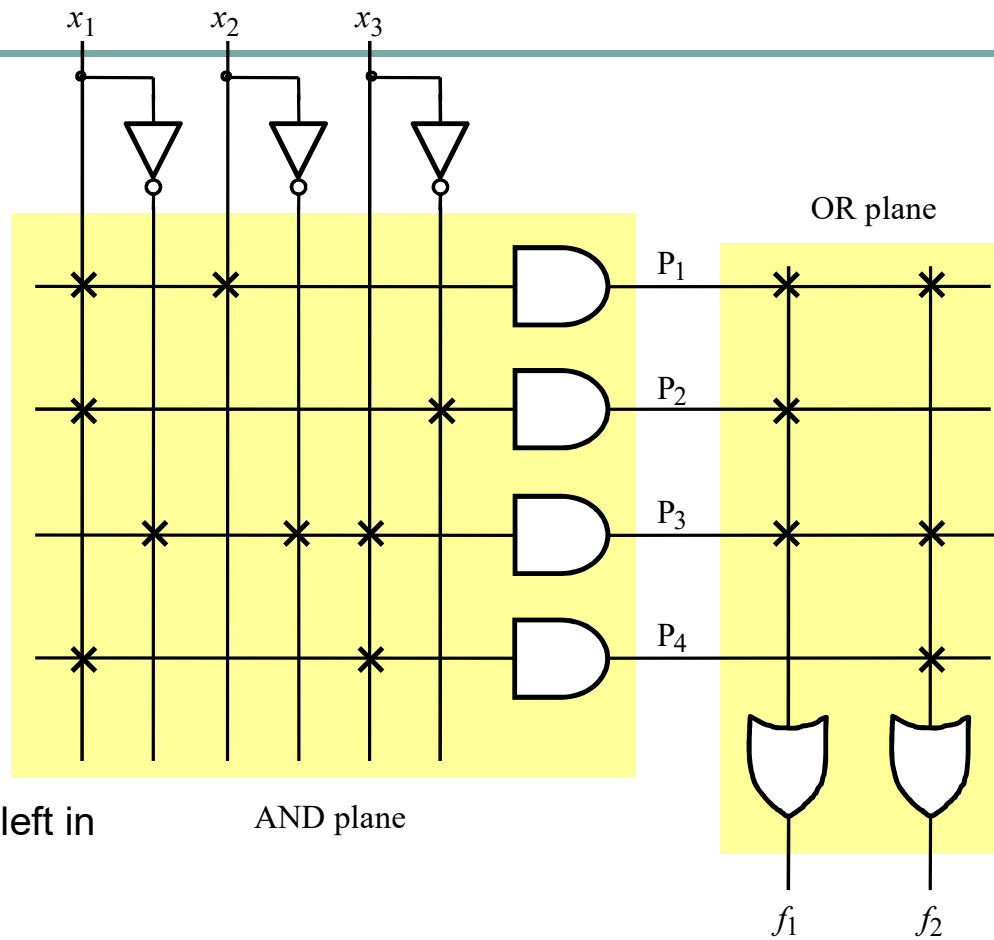

x marks the connections left in place after programming

AND plane

OR plane

f_1

f_2

Limitations of PLAs

- PLAs come in various sizes
 - *Typical size is 16 inputs, 32 product terms, 8 outputs*
 - Each AND gate has large fan-in → this limits the number of inputs that can be provided in a PLA
 - 16 inputs → $2^{16} = 65536$ possible input combinations; only 32 permitted (since 32 AND gates) in a typical PLA
 - 32 AND terms permitted → large fan-in for OR gates as well
 - *This makes PLAs slower and slightly more expensive than some alternatives to be discussed shortly*
 - 8 outputs → could have shared minterms, but not required

Design for PLA: Example

- Implement the following functions using PLA

$$\begin{aligned}
 F_0 &= A + B' C' \\
 F_1 &= A C' + A B \\
 F_2 &= B' C' + A B \\
 F_3 &= B' C + A
 \end{aligned}$$

Personality Matrix

Product term	Inputs			Outputs			
	A	B	C	F ₀	F ₁	F ₂	F ₃
A B	1	1	-	0	1	1	0
B C	-	0	1	0	0	0	1
A C	1	-	0	0	1	0	0
B C	-	0	0	1	0	1	0
A	1	-	-	1	0	0	1

Reuse of terms

Input Side:

- 1 = asserted in term
- 0 = negated in term
- = does not participate

Output Side:

- 1 = term connected to output
- 0 = no connection to output



Example: Continued

$$\begin{aligned}
 F_0 &= A + B' C' \\
 F_1 &= A C' + A B \\
 F_2 &= B' C' + A B \\
 F_3 &= B' C + A
 \end{aligned}$$

Personality Matrix





Product term	Inputs			Outputs			
	A	B	C	F ₀	F ₁	F ₂	F ₃
AB	1	1	-	0	⊕	⊕	0
$\overline{B}C$	-	0	1	0	0	0	1
$A\overline{C}$	1	-	0	0	1	0	0
$\overline{B}C$	-	0	0	⊕	0	⊕	0
A	1	-	-	⊕	0	0	⊕

Reuse of terms

 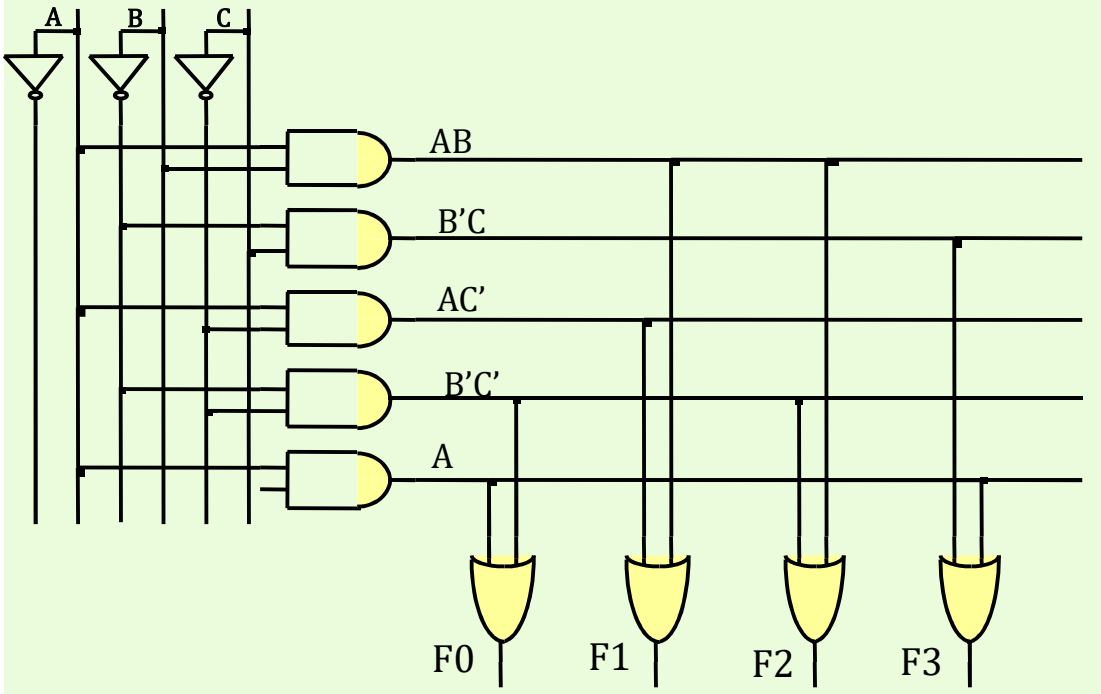

BCD to Gray Code Converter

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	1	1	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

 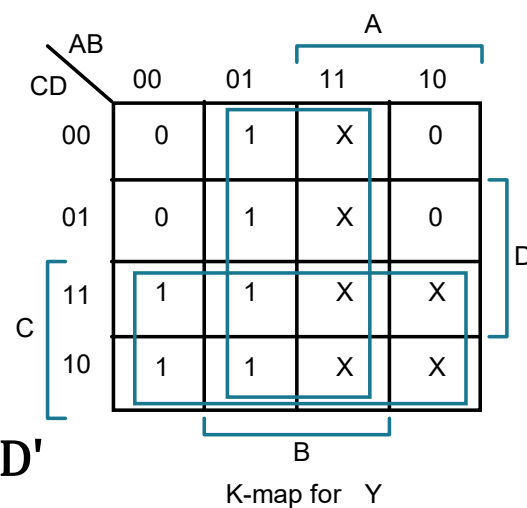  

Minimized Functions:

$$W = A + BD + BC$$

$$X = BC'$$


$$Y = B + C$$

$$Z = A'B'C'D + BCD + AD' + B'CD'$$


4 product terms per each OR gate

Product terms cannot be shared !

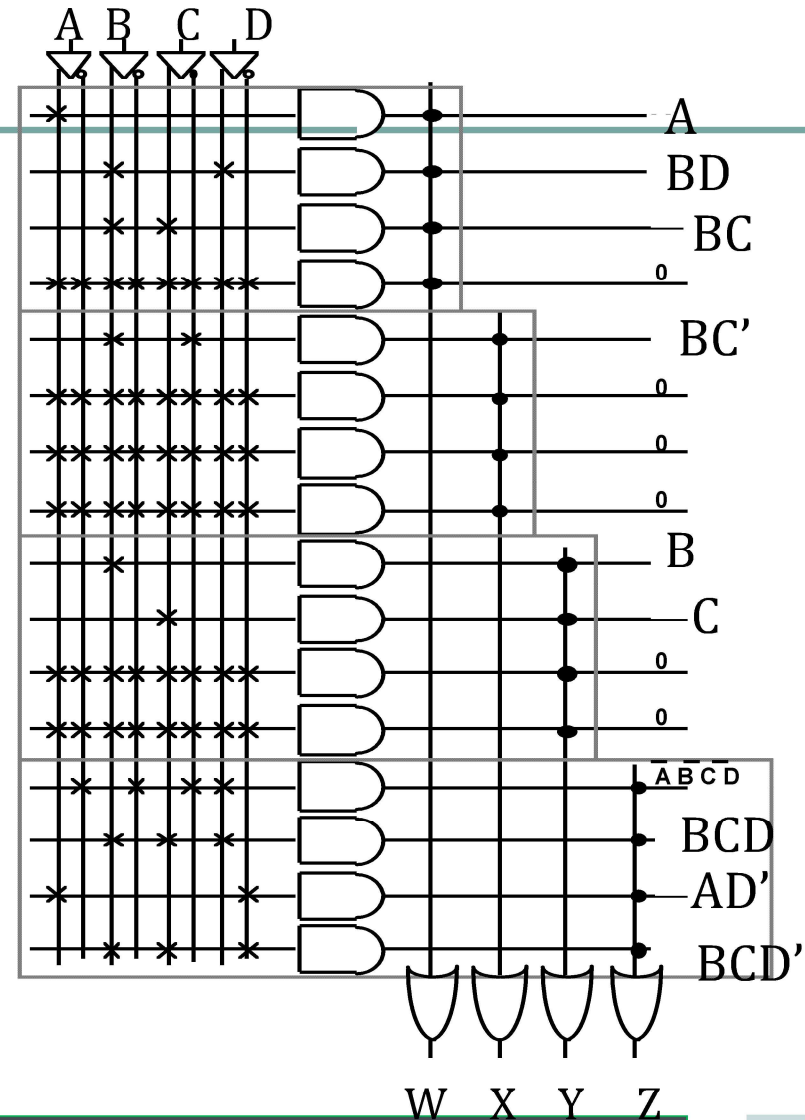PLA achieves higher flexibility at the cost of lower speed!



Array Logic

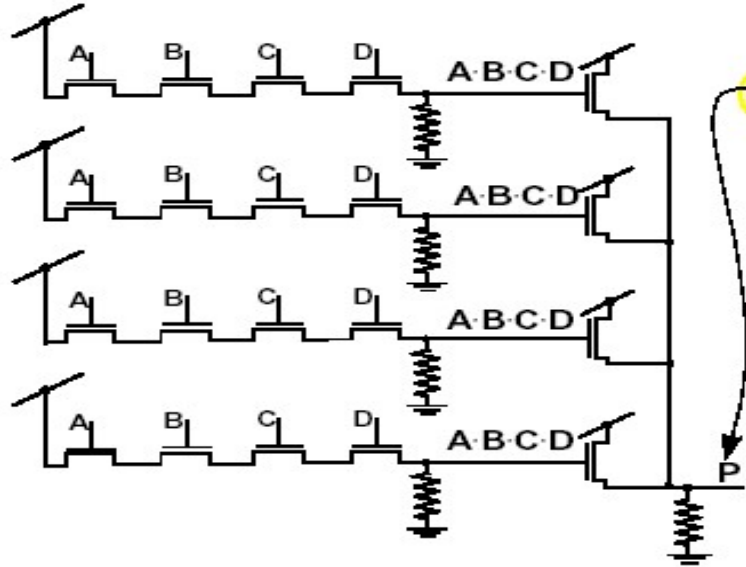


Combine the AND and OR logic

$$P = A \cdot B \cdot C \cdot D + A \cdot B \cdot C \cdot D + A \cdot B \cdot C \cdot D + A \cdot B \cdot C \cdot D$$

A Fuse Programmed Logic Array

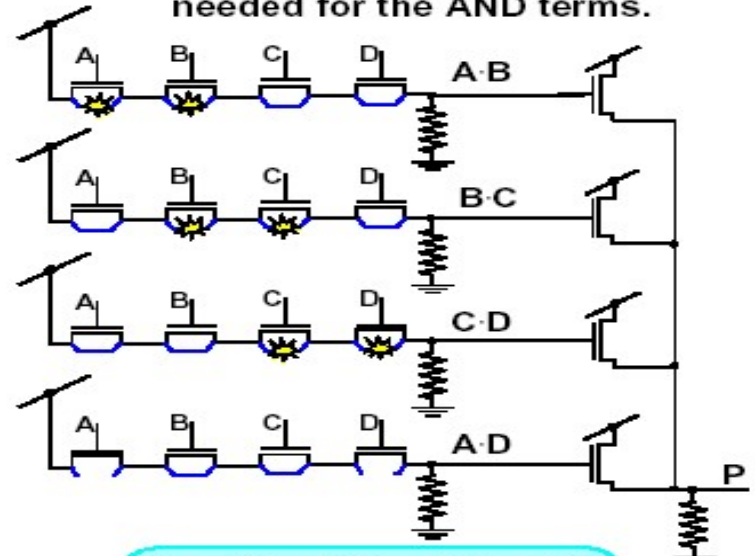
Program the logic
Short all transistors with fuses.
Remove shorts from transistors
needed for the AND terms.




$$P = A \cdot B + B \cdot C + C \cdot D + A \cdot D$$

Fuse Programming

Start with all transistors shorted.

 


Programmable Logic Array (PLA)

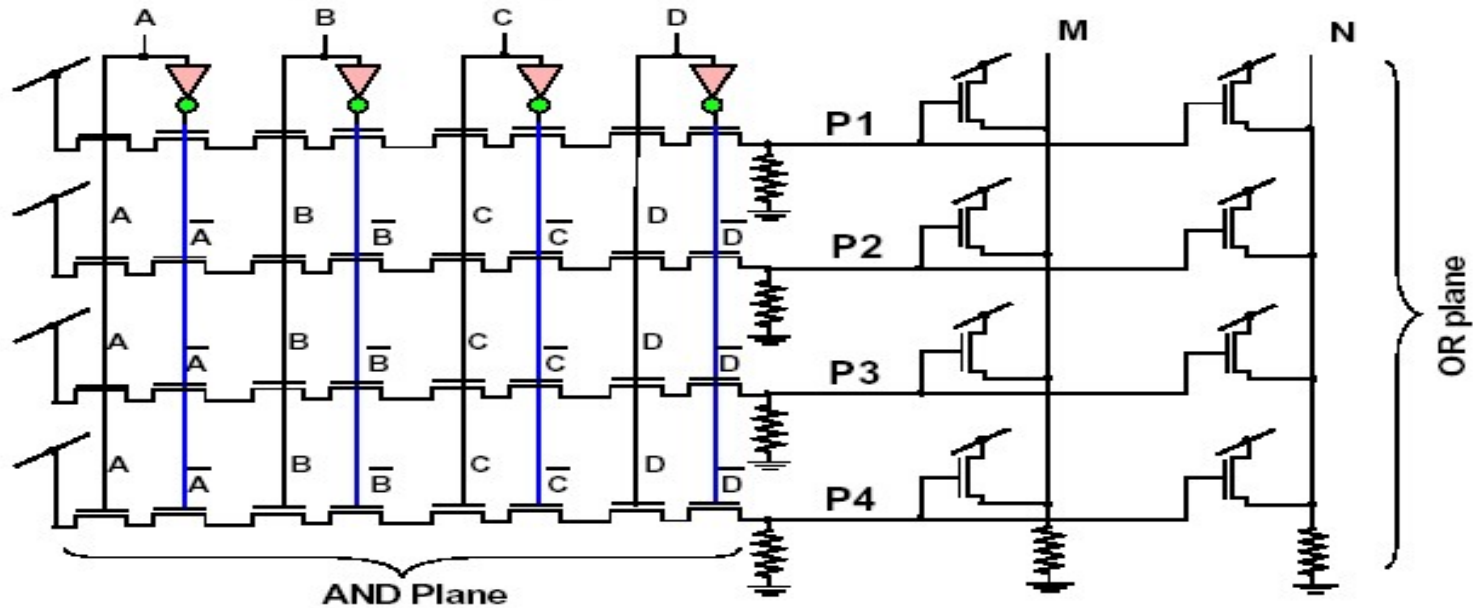


Two outputs M and N
 Can implement two Σ of Π functions
 with 4 inputs which includes x and \bar{x}
 and with 4 product terms, P1, P2, P3 and P4.

Use the simple symbol for logic design

 


Programming the PLA

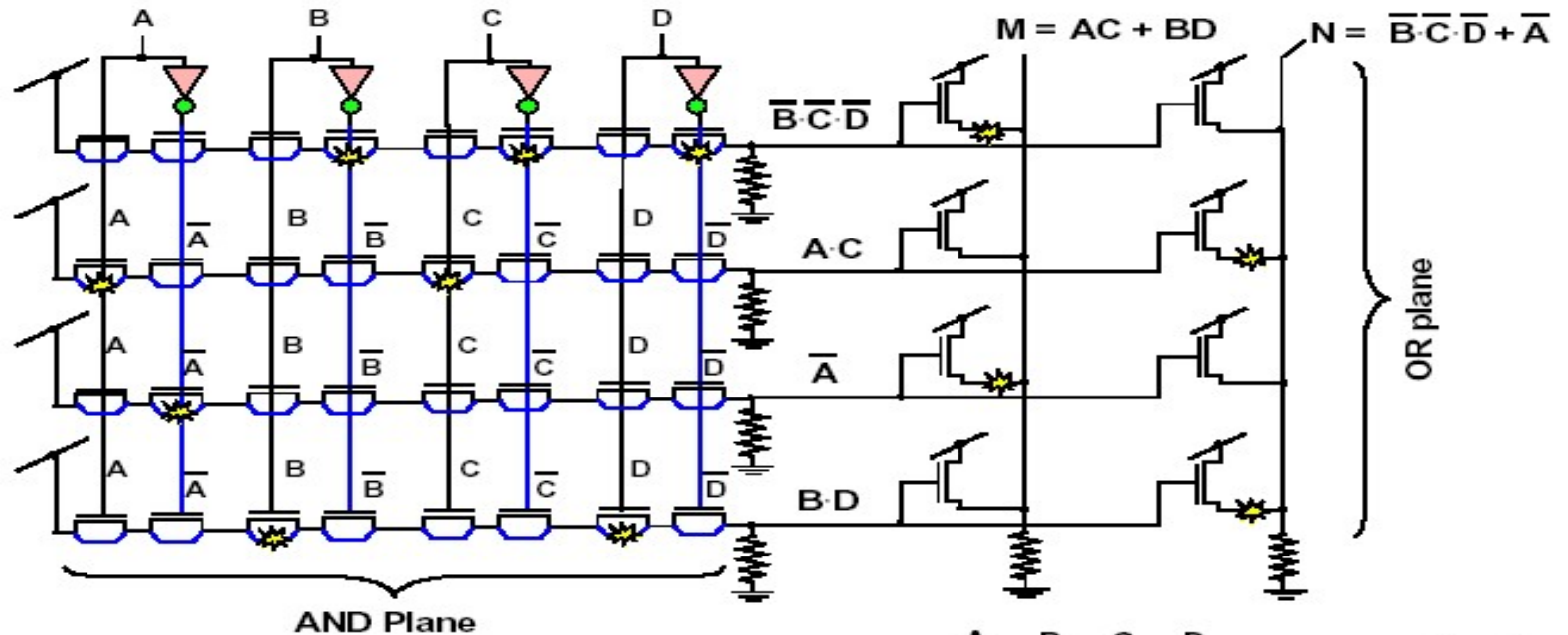

AND Plane
Blow fuses for letters you want in the AND term


OR Plane
Blow fuses to remove unwanted ORs

 Symbolic PLA
Put an \times where you want a connection




Programmable Array Logic (PAL)

 - Also used to implement circuits in SOP form
- The connections in the AND plane are programmable
- The connections in the OR plane are NOT programmable




$$f_1 = x_1x_2x_3' + x_1'x_2x_3$$

$$f_2 = x_1'x_2' + x_1x_2x_3$$

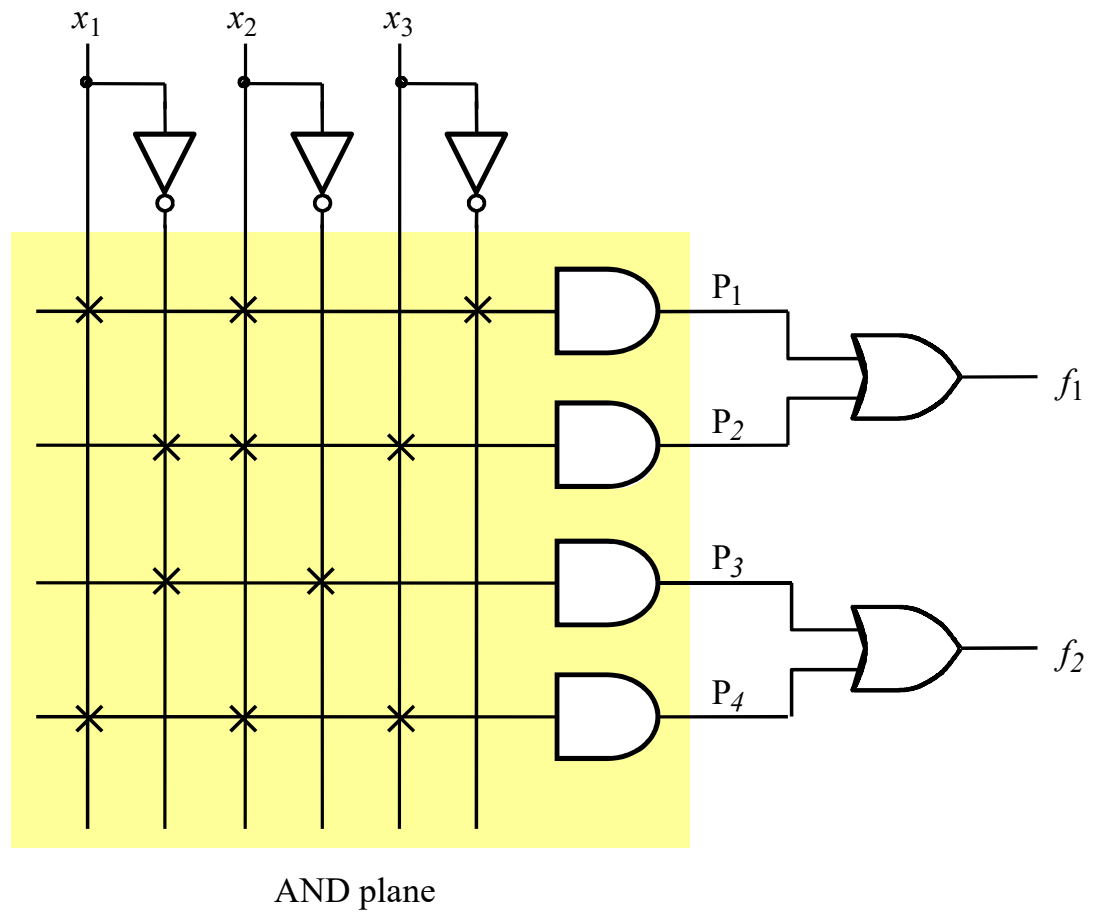

PAL

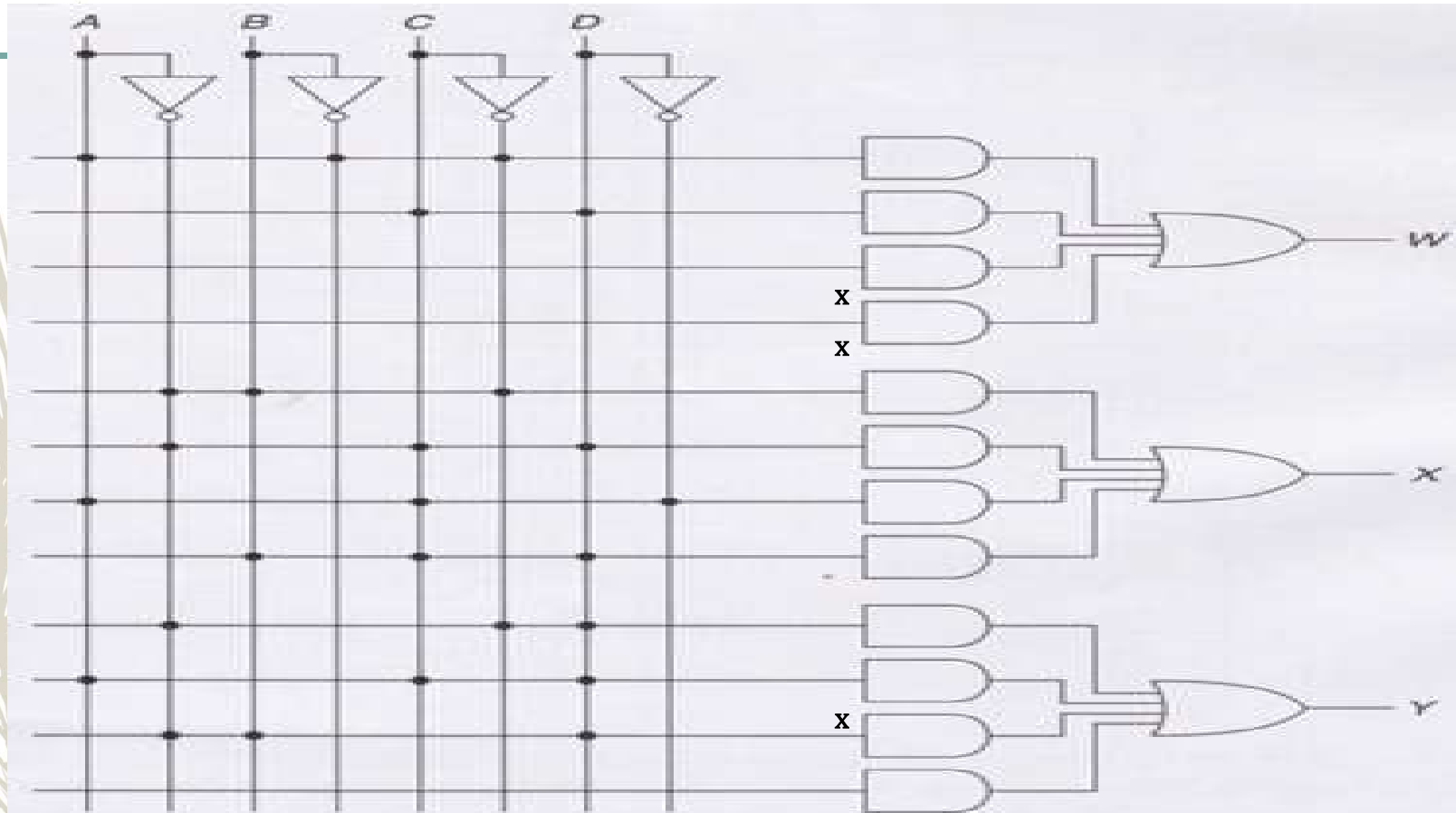

$$W = AB' C + CD$$

$$X = A' BC + A' CD + ACD + BCD$$

$$Y = A' C D + ACD + A' BD$$


Department of Electronics and Communication Engineering, VBIT

VIDYA SAGAR P

Comparing PALs and PLAs


- PALs have the same limitations as PLAs (small number of allowed AND terms) plus they have a fixed OR plane → less flexibility than PLAs
- PALs are simpler to manufacture, cheaper, and faster (better performance)
- PALs also often have extra circuitry connected to the output of each OR gate
 - *The OR gate plus this circuitry is called a macrocell*

Macro cell

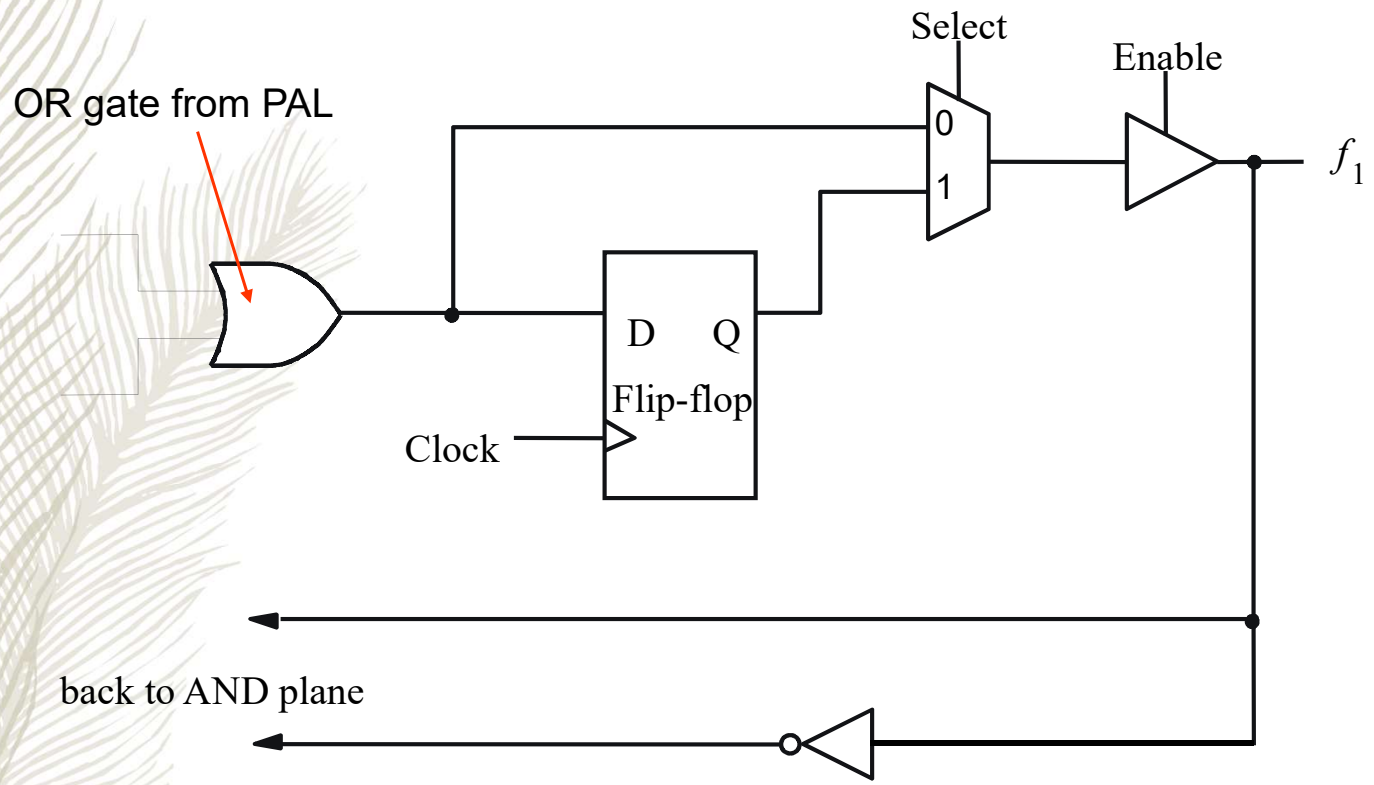

Macrocell Functions

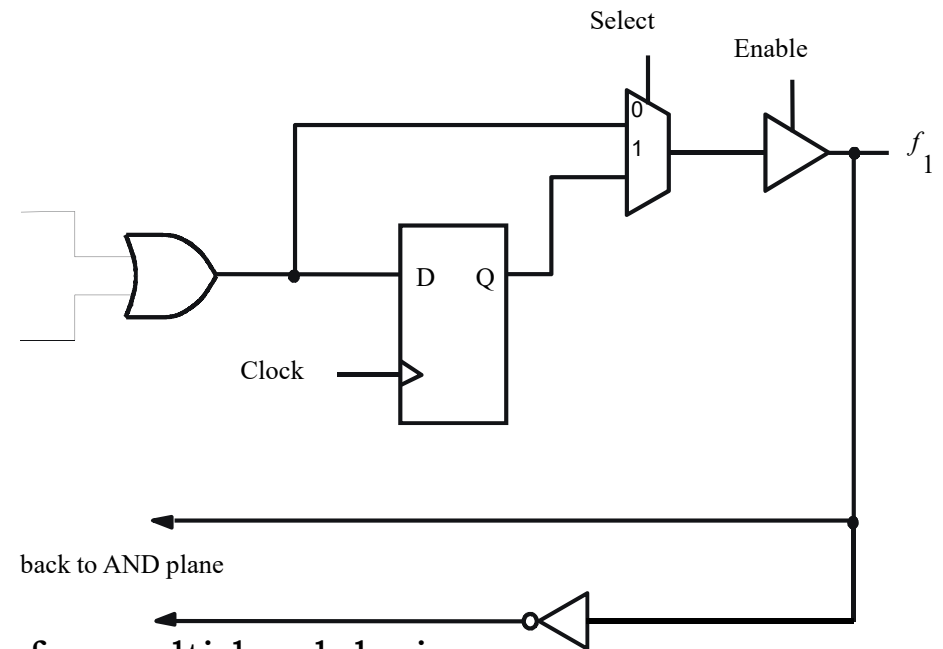
- Enable = 0 can be used to allow the output pin for f_1 to be used as an additional input pin to the PAL
- Enable = 1, Select = 0 is normal for typical PAL operation
- Enable = Select = 1 allows the PAL to synchronize the output changes with a clock pulse
- The feedback to the AND plane provides for multi-level design



Multi-Level Design with PALs

➤ $f = A'BC + A'B'C' + ABC' + AB'C = A'g + Ag'$

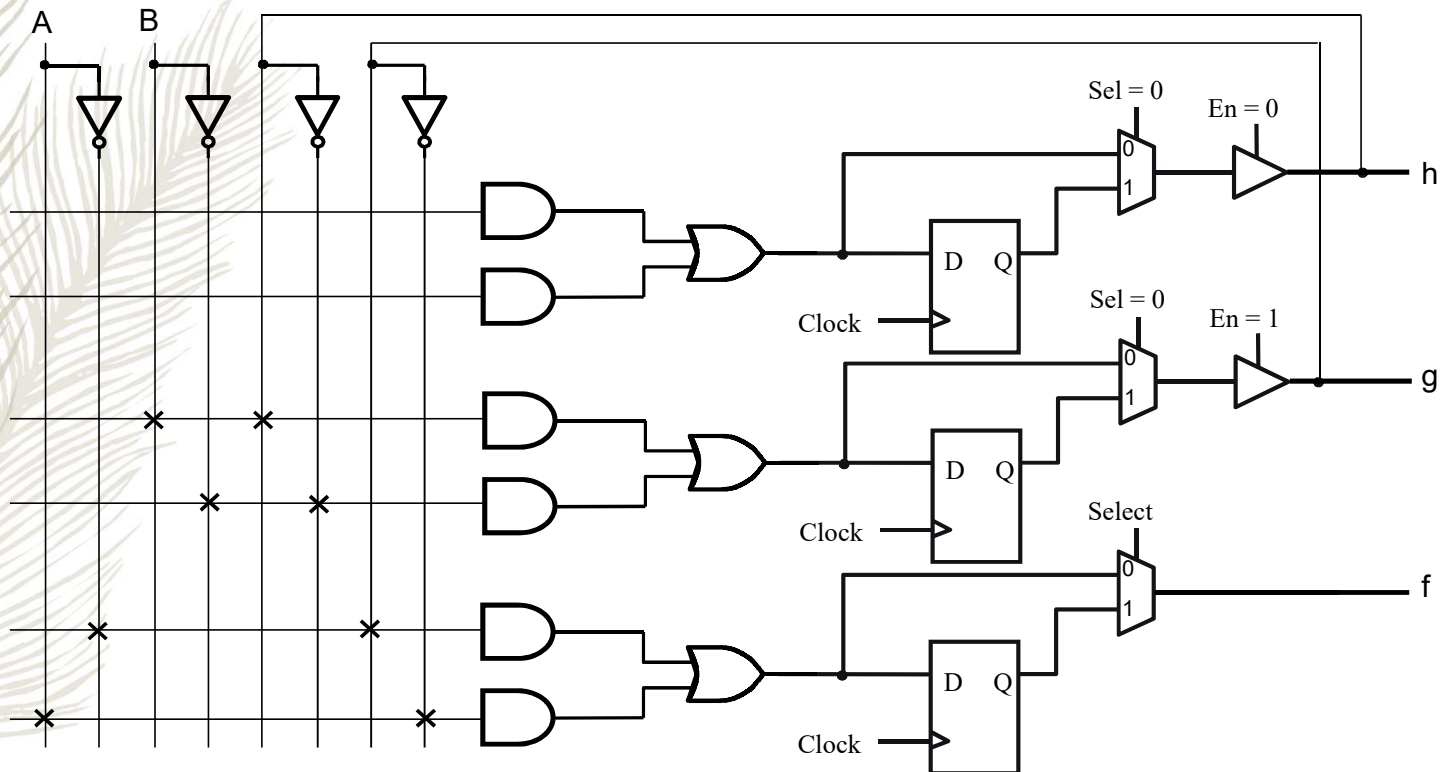➤ where $g = BC + B'C'$ and $C = h$ below



Programming SPLDs

- PLAs, PALs, and ROMs are also called SPLDs – Simple Programmable Logic Devices
- SPLDs must be programmed so that the switches are in the correct places
 - *CAD tools are usually used to do this*
 - A fuse map is created by the CAD tool and then that map is downloaded to the device via a special programming unit
 - *There are two basic types of programming techniques*
 - Removable sockets on a PCB
 - In system programming (ISP) on a PCB
 - *This approach is not very common for PLAs and PALs but it is quite common for more complex PLDs*


– An SPLD Programming Unit



– The SPLD is removed from the PCB, placed into the unit and programmed there


➤ Removable SPLD Socket Package

- PLCC (plastic-leaded chip carrier)

 

➤ In System Programming (ISP)

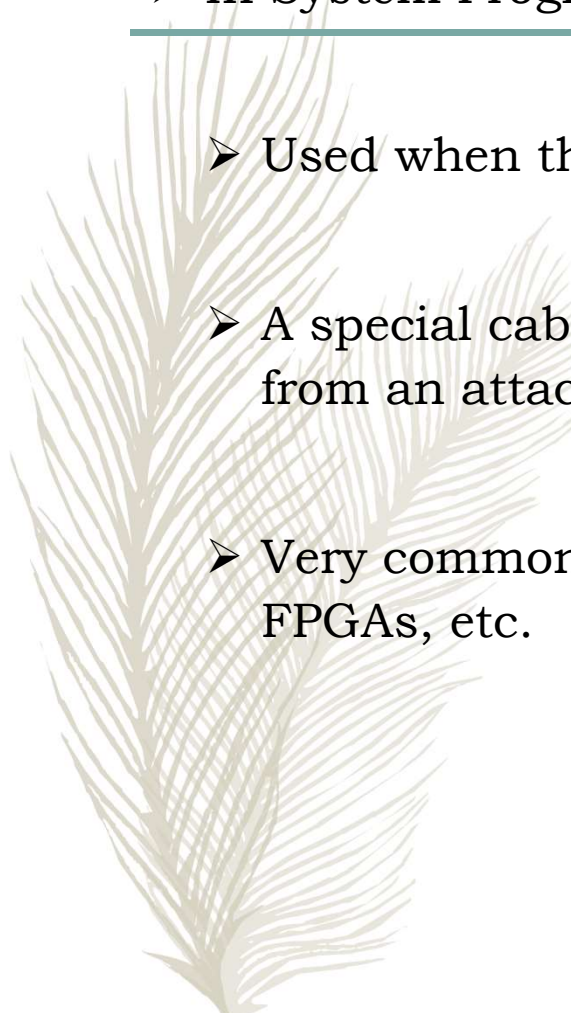- Used when the SPLD cannot be removed from the PCB
- A special cable and PCB connection are required to program the SPLD from an attached computer
- Very common approach to programming more complex PLDs like CPLDs, FPGAs, etc.



FPGA AND CPLD


- FPGA - Field-Programmable Gate Array.
- CPLD - Complex Programmable Logic Device
- FPGA and CPLD is an advance PLD.
- Support thousands of gate where as PLD only support hundreds of gates.



CPLD


- Complex Programmable Logic Devices (CPLD)
- SPLDs (PLA, PAL) are limited in size due to the small number of input and output pins and the limited number of product terms
 - *Combined number of inputs + outputs < 32 or so*
- CPLDs contain multiple circuit blocks on a single chip
 - *Each block is like a PAL: PAL-like block*
 - *Connections are provided between PAL-like blocks via an interconnection network that is programmable*
 - *Each block is connected to an I/O block as well*

Structure of a CPLD

 


Internal Structure of a PAL-like Block

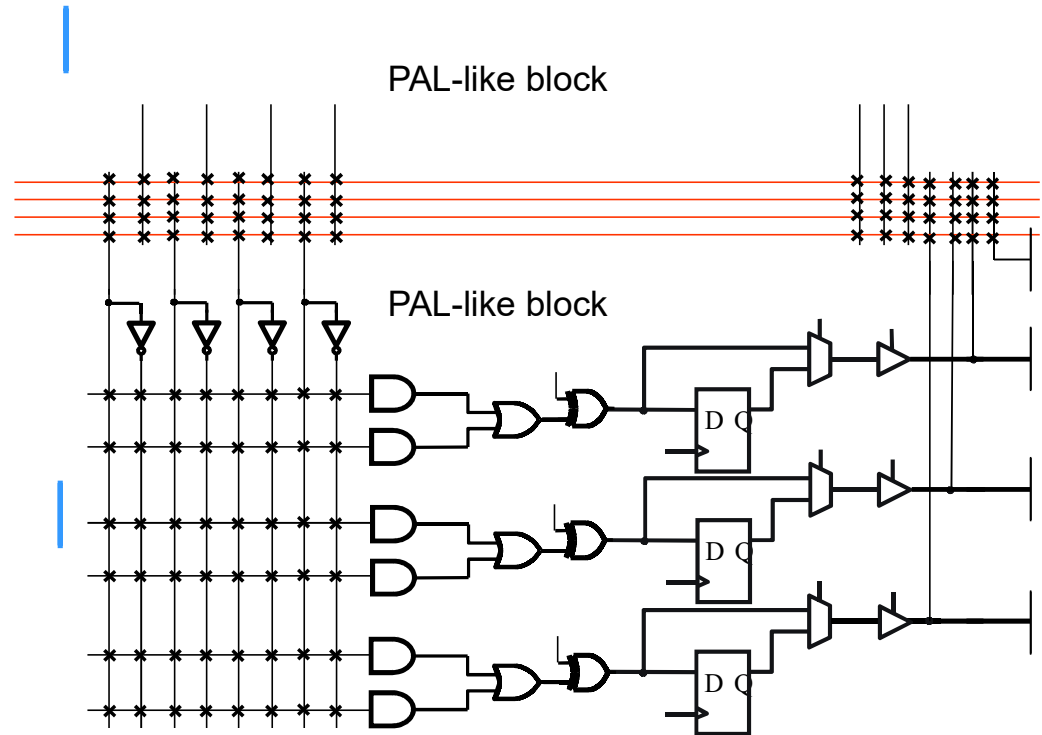- Includes macrocells
 - Usually about 16 each
- Fixed OR planes
 - OR gates have fan-in between 5-20
- XOR gates provide negation ability
 - XOR has a control input



Programming a CPLD

 
- CPLDs have many pins – large ones have > 200
 - *Removal of CPLD from a PCB is difficult without breaking the pins*
 - *Use ISP (in system programming) to program the CPLD*
 - *JTAG (Joint Test Action Group) port used to connect the CPLD to a computer*



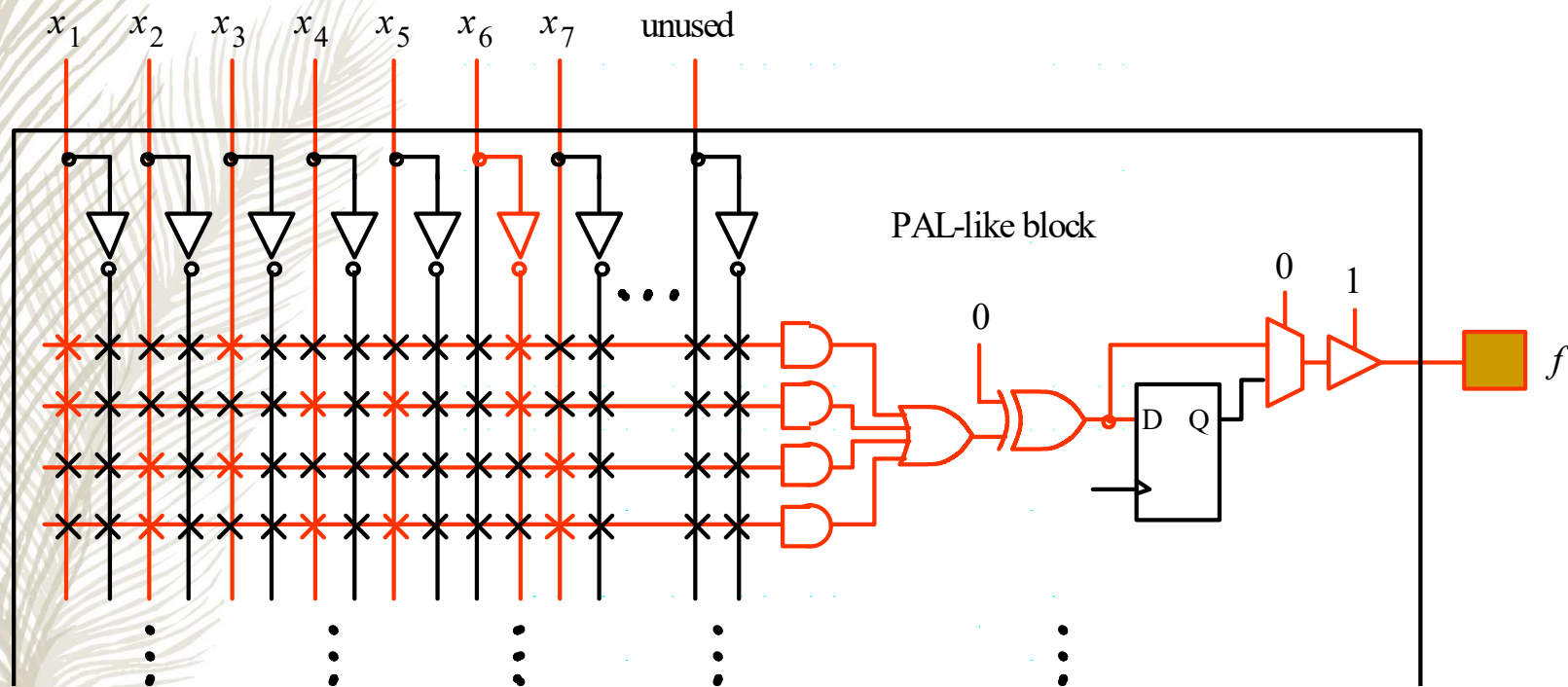Example CPLD

➤ Use a CPLD to implement the function


➤ $f = x_1x_3x_6' + x_1x_4x_5x_6' + x_2x_3x_7 + x_2x_4x_5x_7$
(from interconnection wires)



FPGA


- SPLDs and CPLDs are relatively small and useful for simple logic devices
 - *Up to about 20000 gates*
- Field Programmable Gate Arrays (FPGA) can handle larger circuits
 - *No AND/OR planes*
 - *Provide logic blocks, I/O blocks, and interconnection wires and switches*
 - *Logic blocks provide functionality*
 - *Interconnection switches allow logic blocks to be connected to each other and to the I/O pins*

Structure of an FPGA

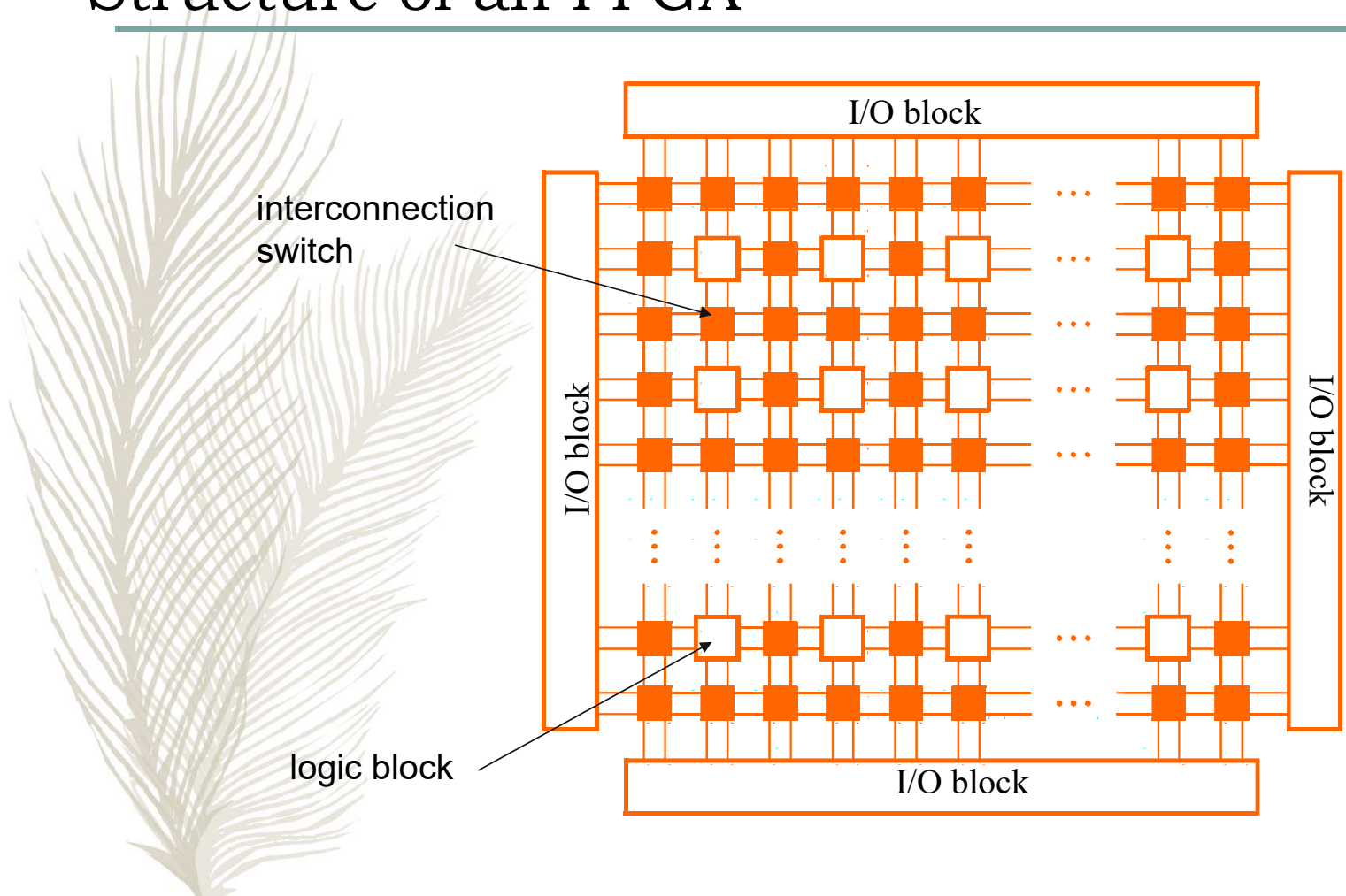

LUTs

 - Logic blocks are implemented using a lookup table (LUT)
- *Small number of inputs, one output*
- *Contains storage cells that can be loaded with the desired values*
- *A 2 input LUT uses 3 MUXes to implement any desired function of 2 variables*
- *Shannon's expansion at work!*




Example 2 Input LUT

x_1	x_2	f
0	0	1
0	1	0
1	0	0
1	1	1


$f = x_1'x_2' + x_1x_2$, or using Shannon's expansion:
 
$$\begin{aligned} f &= x_1'(x_2') + x_1(x_2) \\ &= x_1'(x_2'(1) + x_2(0)) + x_1(x_2'(0) + x_2(1)) \end{aligned}$$



3 Input LUT

 - 7 2x1 MUXEs and 8 storage cells are required
- Commercial LUTs have 4-5 inputs, and 16-32 storage cells



Programming an FPGA

- ISP method is used
- LUTs contain volatile storage cells
 - *None of the other PLD technologies are volatile*
 - *FPGA storage cells are loaded via a PROM when power is first applied*
- The UP2 Education Board by Altera contains a JTAG port, a MAX 7000 CPLD, and a FLEX 10K FPGA
 - *The MAX 7000 CPLD chip is EPM7128SLC84-7*
 - *EPM7 → MAX 7000 family; 128 macrocells; LC84 → 84 pin PLCC package; 7 → speed grade*

Example FPGA


➤ Use an FPGA with 2 input LUTs to implement the function $f =$

$$x_1x_2 + x_2'x_3$$

➤ $f_1 = x_1x_2$

➤ $f_2 = x_2'x_3$

- $f = f_1 + f_2$

 


Another Example FPGA

- Use an FPGA with 2 input LUTS to implement the function
- $f = x_1x_3x_6' + x_1x_4x_5x_6' + x_2x_3x_7 + x_2x_4x_5x_7$
 - *Fan-in of expression is too large for FPGA (this was simple to do in a CPLD)*
 - *Factor f to get sub-expressions with max fan-in = 2*
 - $f = x_1x_6'(x_3 + x_4x_5) + x_2x_7(x_3 + x_4x_5)$
 $= (x_1x_6' + x_2x_7)(x_3 + x_4x_5)$
 - *Could use Shannon's expansion instead*
 - Goal is to build expressions out of 2-input LUTs




FPGA Implementation

➤ $f = (x_1x_6' + x_2x_7)(x_3 + x_4x_5)$

 

Standard Cells

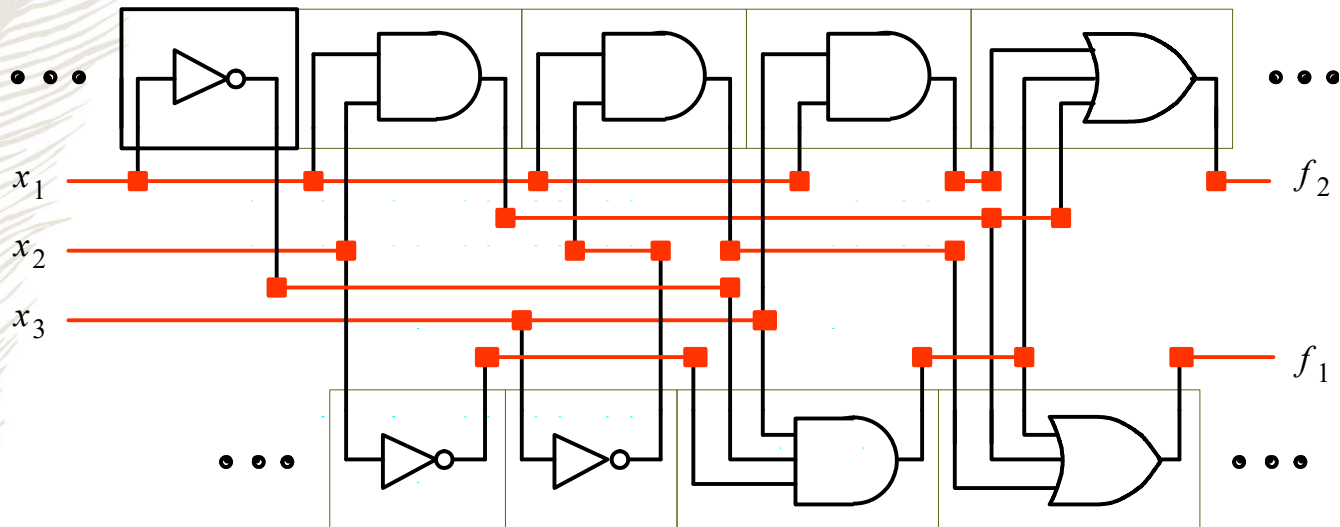
- Rows of logic gates can be connected by wires in the *routing channels*
 - Designers (via CAD tools) select prefab gates from a library and place them in rows
 - Interconnections are made by wires in routing channels
 - Multiple layers may be used to avoid short circuiting
 - A hard-wired connection between layers is called a *via*



Example: Standard Cells


➤ $f_1 = x_1x_2 + x_1'x_2'x_3 + x_1x_3'$

➤ $f_2 = x_1x_2 + x_1'x_2'x_3 + x_1x_3$

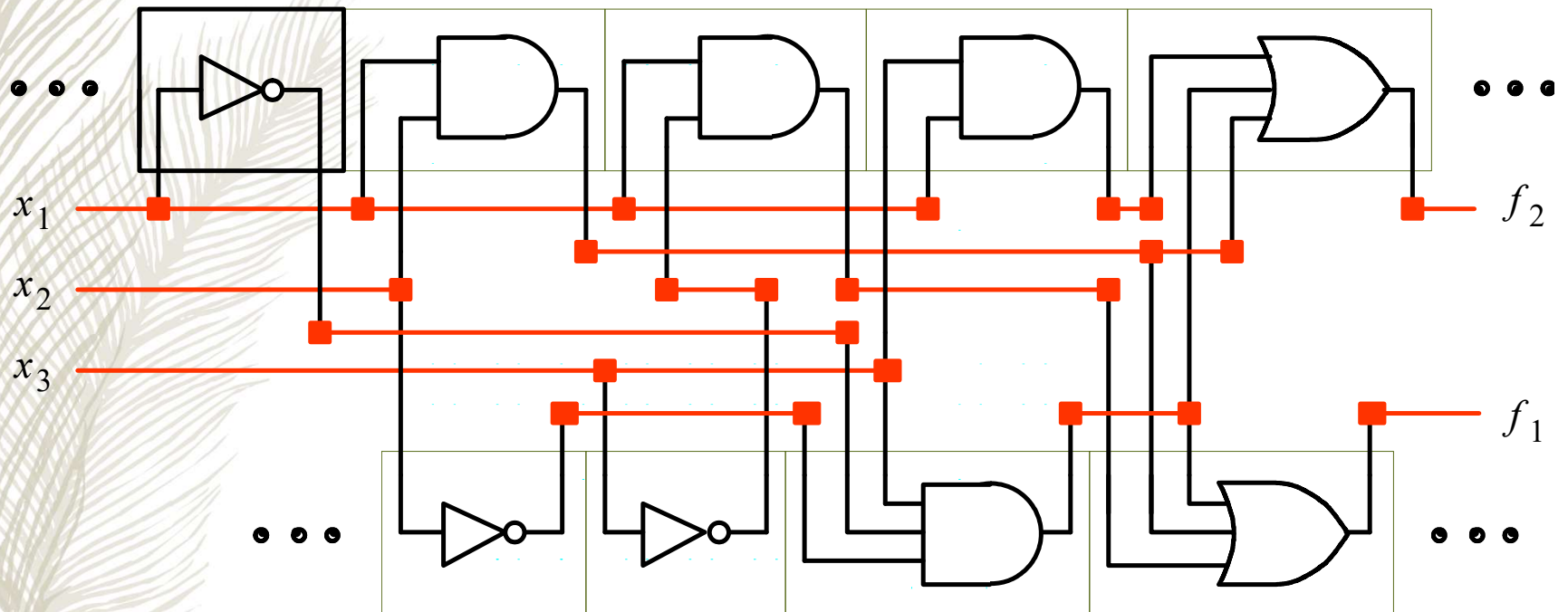


Sea of Gates Gate Array

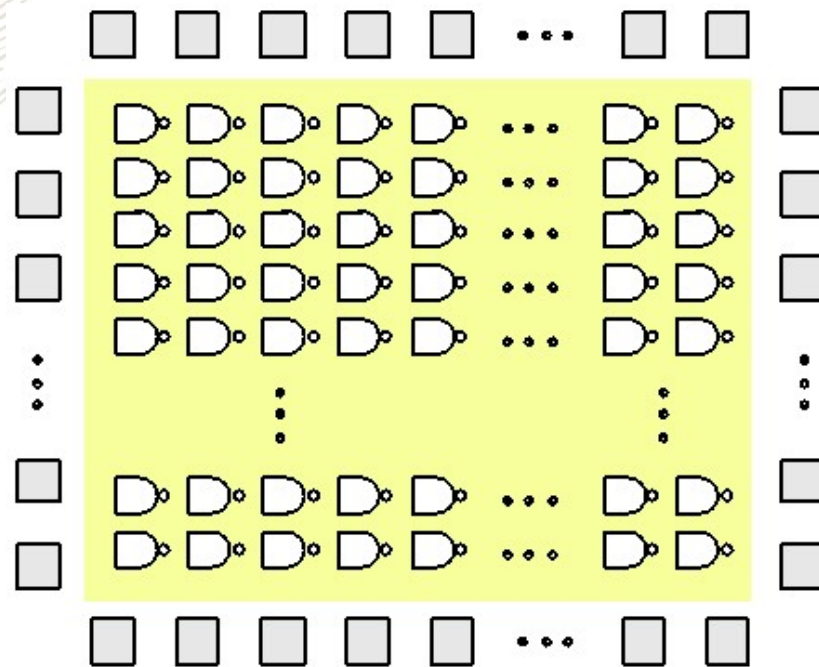- A Sea of Gates gate array is just like a standard cell except all gates are of the same type
- *Interconnections are run in channels and use multiple layers*
- *Cheaper to manufacture due to regularity*




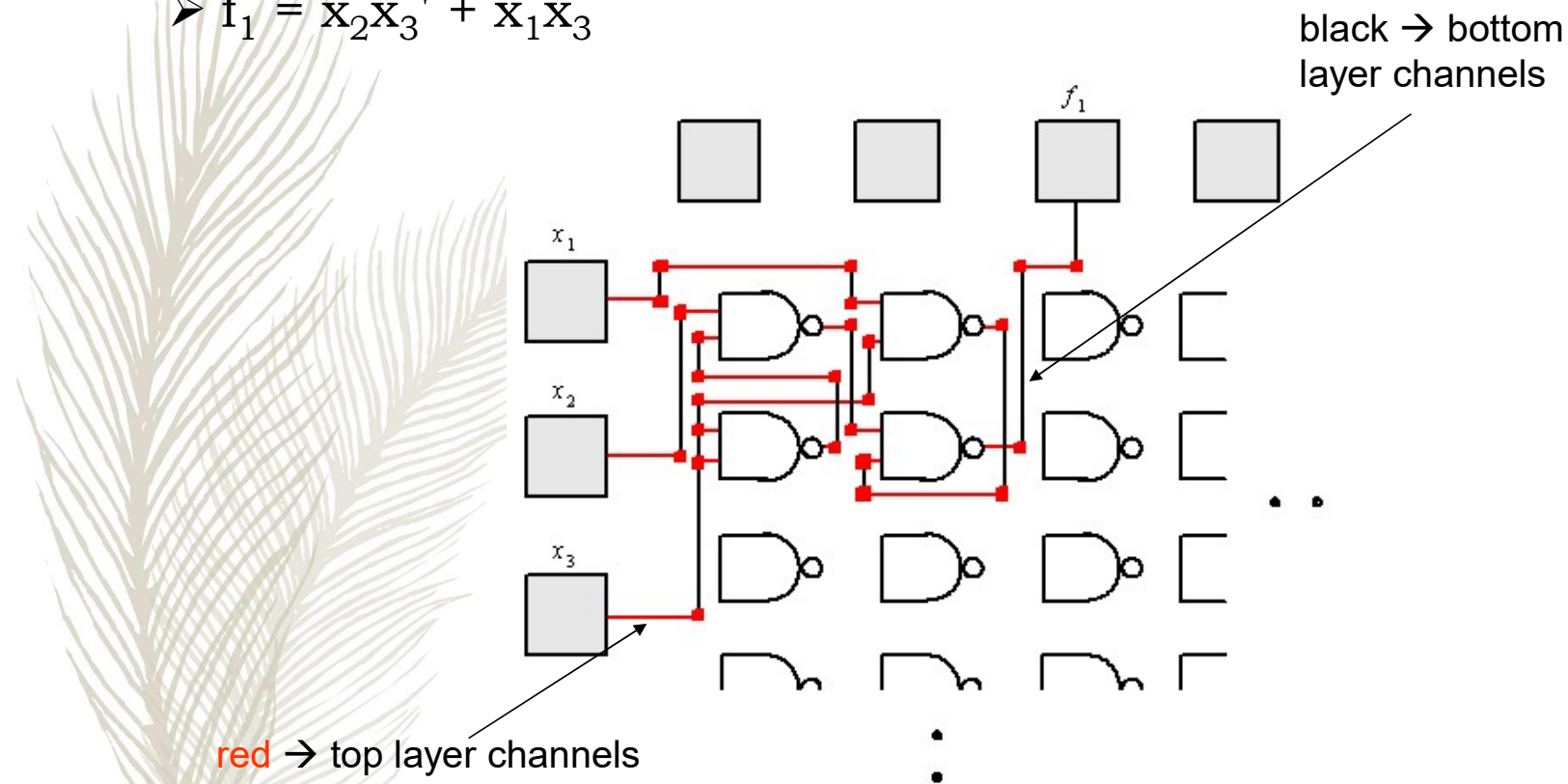Example: Sea of Gates


$$\triangleright f_1 = x_2x_3' + x_1x_3$$




Xilinx Spartan-3E Starter Kit

 

FPGA structure

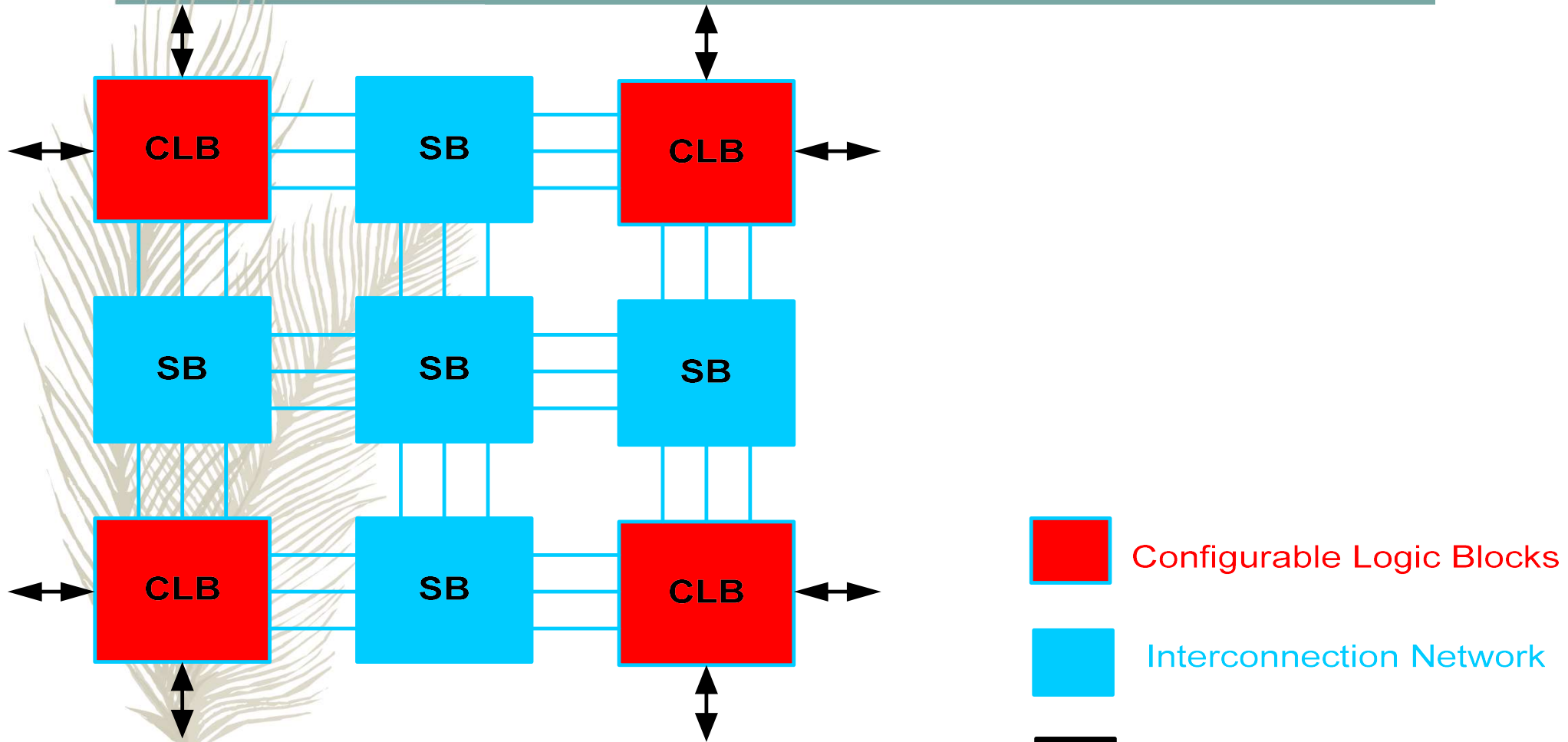


Simplified CLB Structure

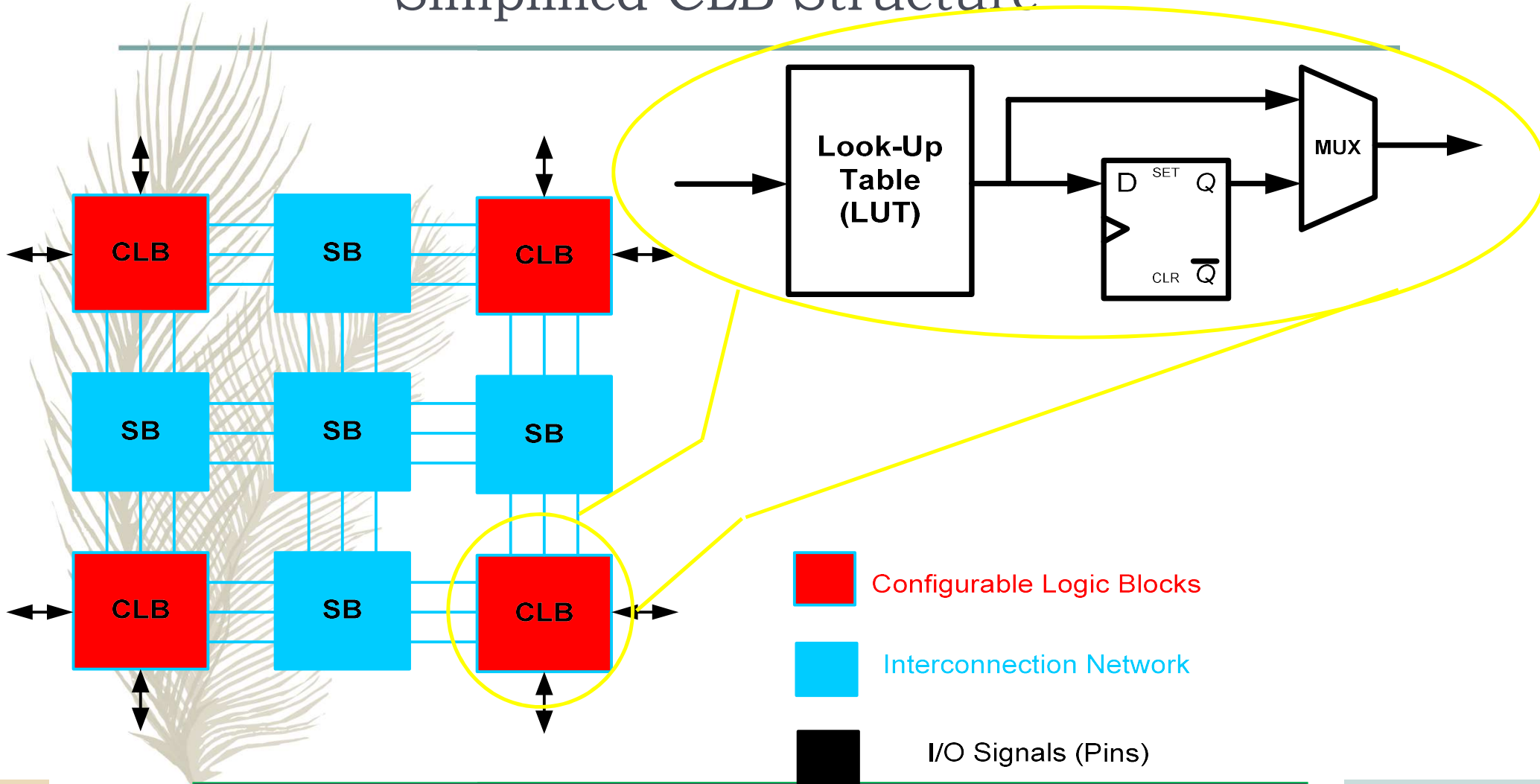


- Configurable Logic Blocks
- Interconnection Network
- I/O Signals (Pins)

Example: 4-input AND gate

 

A	B	C	D	O
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

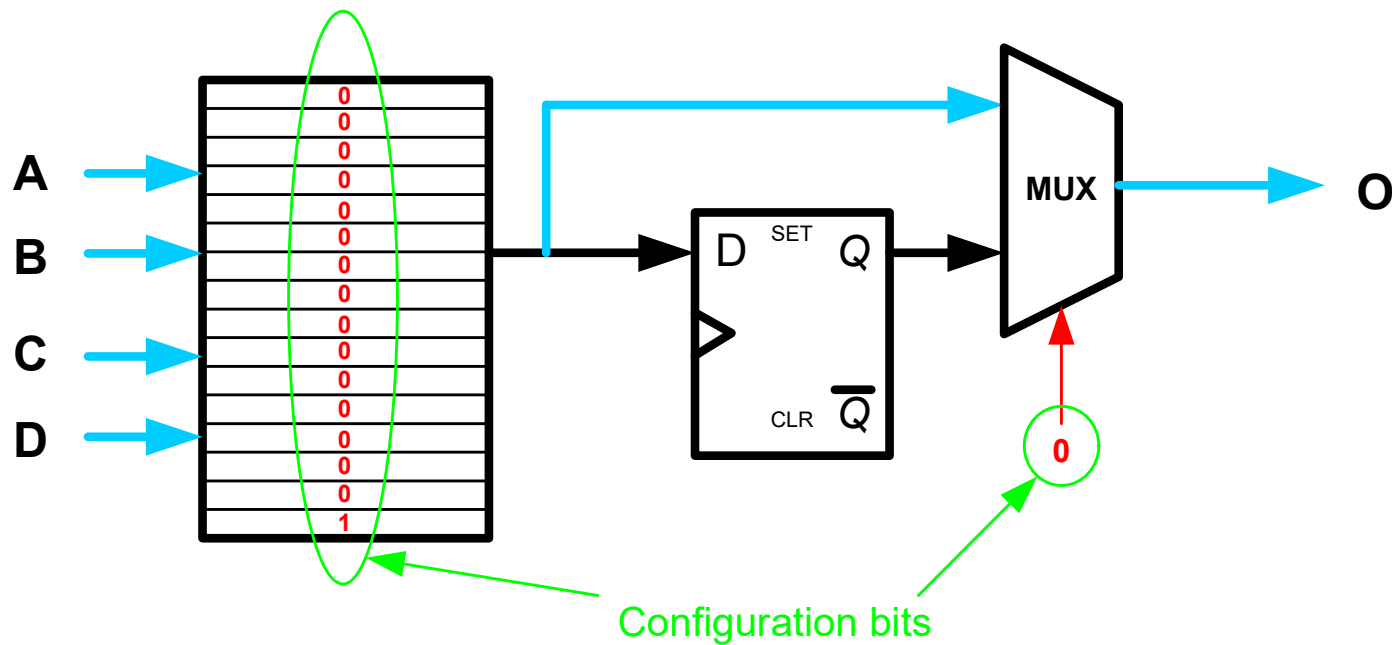

FPGA Advantages

- Long time availability
- Can be updated and upgraded at your customer's site
- Extremely short time to market
- Fast and efficient systems
- Performance gain for software applications
- Real time applications
- Massively parallel data processing

FPGA

- FPGA applications:-
 - DSP
 - Software-defined radio
 - Aerospace
 - Defense system
 - ASIC Prototyping
 - Medical Imaging
 - Computer vision
 - Speech Recognition
 - Cryptography
 - Bioinformatics
 - And others.



CMOS TESTING

Topics

- Need for testing
- Test principles
- Design strategies for test
- Chip level test techniques
- System level test techniques

Need for Testing

- The need of testing is to find out errors in the application. The good reasons of testing are

 - 1) Quality Assurance.
 - 2) Verification and validating the product/application before it goes live in the market.
 - 3) Defect free and user friendly.
 - 4) Meets the requirements.
 - Testing is one of the most expensive parts of chips
 - Logic verification accounts for > 50% of design effort for many chips
 - Debug time after fabrication has enormous opportunity cost
 - Shipping defective parts can sink a company
 - Decreasing feature size increases probability of defects during manufacturing process.
 - imperfections in chip fabrication may lead to manufacturing defects
- The manufacturing yield (Y) depends on the used technology, the silicon area and the layout design.
- $$Y = \text{no of acceptable parts} / \text{total no of fabricated parts}$$
- Example: Intel FDIV bug (1994)
 - Logic error not caught until > 1M units shipped * Recall cost \$450M (!!!)

Rule of Ten

- Rule of Ten: cost to detect faulty IC increases by an order of magnitude as we move from:
 - ❖ device →PCB →system →field operation– Testing performed at all of these levels
- Cost to detect a fault (per chip)
 - ❖ Wafer: \$0.01-\$0.1
 - ❖ Packaged chip: \$0.1-\$1
 - ❖ Board: \$1-\$10
 - ❖ System: \$10-\$100
 - ❖ Field: \$100-1000

Role of Testing

Detection: Determination whether or not the device under test (DUT) has some fault.


Diagnosis: Identification of a specific fault that is present on DUT.

Device characterization: Determination and correction of errors in design and/or test procedure.

Failure mode analysis (FMA): Determination of manufacturing process errors that may have caused defects on the DUT.

- ❖ **Defects** : are circuit failures and malfunctions due to the manufacturing process(eg:short circuits opens).
- ❖ **Faults** :model the influence of defects on the circuit operation (e.g. a line (node) is permanently stuck-at“1” or “0”).
- ❖ **Errors:** are the incorrect logic responses of the circuit under the presence of faults.

Classification of tests

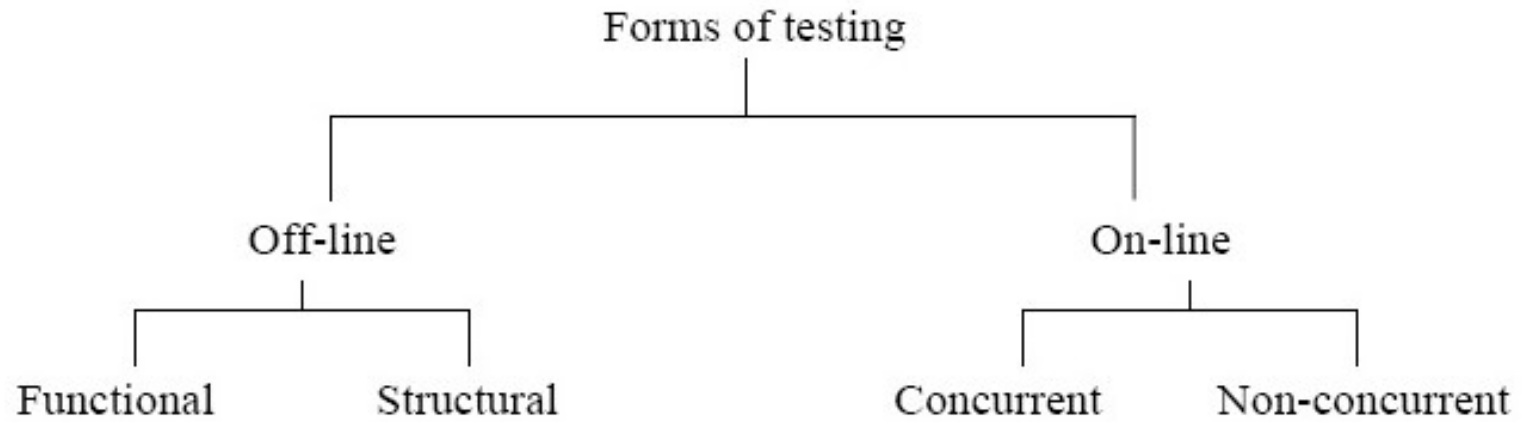

Off Chip and On Chip Testing

Off chip testing: The test procedures are applied by external to the chip test equipment's (Automatic Test Equipment–ATE or Tester).

On chip testing: Embedded, on-chip, resources are provided in order to support the testing procedures.

- ❖ **On-line testing:** Testing procedures are applied in the field of operation.
Concurrent testing: Testing is performed concurrently with the circuit operation in the field, during the normal mode.
- ❖ **Periodic testing:** Testing is performed periodically, during idle times of the circuit operation.
- **Off-line testing:** Testing procedures are applied out of the VLSI Testing field of operation, usually after fabrication (manufacturing testing).

Logic Verification

- Does the chip simulate correctly?
 - Usually done at HDL level
 - Verification engineers write test bench for HDL
 - *Can't test all cases*
 - *Look for corner cases*
 - *Try to break logic design*
- Ex: 32-bit adder
 - Test all combinations of corner cases as inputs:
 - *0, 1, 2, 2³¹-1, -1, -2³¹, a few random numbers*
 - Good tests require ingenuity

Manufacturing Test


- A speck of dust on a wafer is sufficient to kill chip
- Yield of any chip is $< 100\%$
 - Must test chips after manufacturing before delivery to customers to only ship good parts
- Manufacturing testers are very expensive
 - Minimize time on tester
 - Careful selection of test vectors

Defects: layer-to-layer shorts, discontinuous wires
thin-oxide shorts to substrate or well


Faults: nodes shorted to power or ground (stuck-at)
nodes shorted to each other (bridging)
inputs floating, outputs disconnected (stuck-open)




Manufacturing Failures

 


Metal 1 Shelving

 

 
**Metal 5 film particle
(bridging defect)**




Open defect

 


**Spongy Via2
(Infant mortality)**

 

 **Metal 5 blocked etch
(patterning defect)**



**Spot defects
"Co" Defect under Gate**

 

**Metal 1 missing pattern
(open at contact)**

SEM images courtesy Intel Corporation

Fault types and Models

- Errors :- Permanent- Intermittent- Transient
- Faults :- Physical- Logical

The physical defects can cause electrical faults and logical faults.

The **electrical faults** include: Shorts (bridging faults) & opens-Transistor stuck-on, stuck-open-Resistive shorts and opens-Excessive change in threshold voltage-Excessive steady-state currents

The **logical faults** include: Logical stuck-at-0 or stuck-at-1-Slower transition-AND-bridging, OR bridging

Electrical Faults : Stuck-On, Stuck-Open

Test Process

➤ The testing problem

Given a set of faults in the circuit under test (or device under test), how do we obtain a certain (small) number of test patterns which guarantees a certain (high) fault coverage?

- Test process
- What faults to test? (***fault modeling***)
- How are test pattern obtained? (***test pattern generation***)
- How is test quality (fault coverage) measured?
(***fault simulation***)?
- How are test vectors applied and results evaluated?
(***ATE/BIST***)

Why Model Faults ?


- Identifies target faults
 - Model faults most likely to occur
- Limits the scope of test generation
 - Create tests only for the modeled faults
- Makes analysis possible
 - Associate specific defects with specific test patterns
- Makes test effectiveness measurable by experiments
 - Fault coverage can be computed for specific test patterns to reflect its effectiveness

Fault Nature & Fault Duration

- **Logical fault** : One that causes the logic function of a circuit element to be changed to some other function
- **Parametric fault** : One that alters the magnitude of a circuit parameter, causing a change in some factor such as resistance, capacitance, current, etc.
- **Delay fault** : One that relates to circuit delays such as slow gates, usually affecting the timing of the circuit, which may cause hazards, or performance degradation, etc.
- ❖ **Permanent fault** : A lasting fault that is continuous and stable, whose nature does not change before, during, and after testing. E.g., a broken wire, an incorrect bonding, etc.
 - A.k.a hard fault or solid fault
- ❖ **Temporary fault** : A fault that is present only part of the time, occurring at random moments and affecting the system for finite, but unknown, intervals of time
 - Transition fault : Caused by environmental conditions, e.g., cosmic rays, alpha particle, etc. A.k.a. soft error in RAMs
 - Intermittent fault : Caused by non-environmental conditions, e.g., marginal values of component parameters, wear-out, or critical timing

Fault Modeling

 - The effects of physical defects
- Most commonly used fault model: Single stuck-at fault



A s-a-1 B s-a-1 C s-a-1 D s-a-1

A s-a-0 B s-a-0 C s-a-0 D s-a-0

E s-a-1 F s-a-1 G s-a-1

E s-a-0 F s-a-0 G s-a-0

14 faults


➤ Other fault models:

- Break faults, Bridging faults, Transistor stuck-open faults, Transistor stuck-on faults, Delay faults

Fault Coverage (FC)

$$FC = \frac{\text{\# faults detected}}{\text{\# faults in fault list}}$$


Example:

 


6 stuck-at faults
($a_0, a_1, b_0, b_1, c_0, c_1$)

Test	faults detected	FC
{(0,0)}	c_1	16.67%
{(0,1)}	a_1, c_1	33.33%
{(1,1)}	a_0, b_0, c_0	50.00%
{(0,0),(1,1)}	a_0, b_0, c_0, c_1	66.67%
{(1,0),(0,1),(1,1)}	all	100.00%

Wafer Yield (Chip Yield, Yield)

 

Testing and Quality

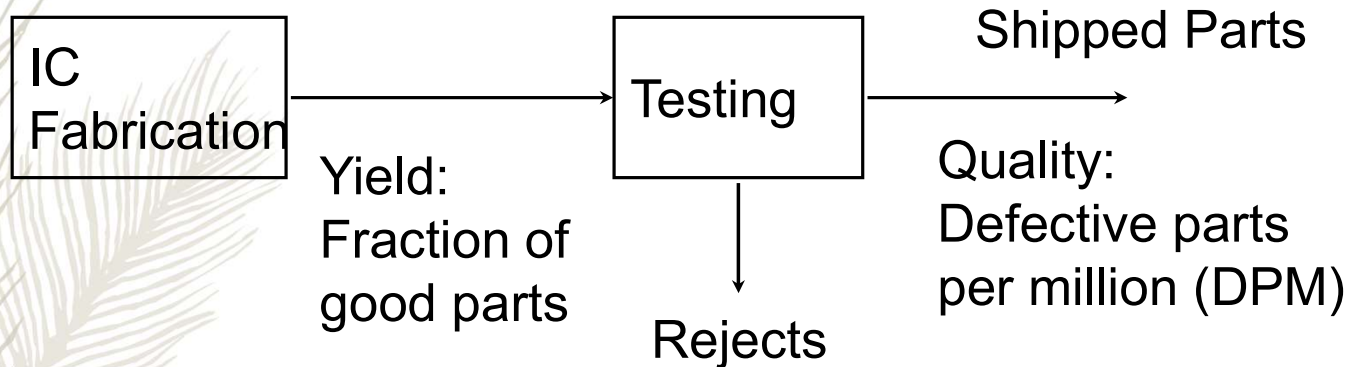

- Quality of shipped parts is a function of yield Y and the test (fault) coverage T
- Defect level (DL, reject rate in textbook): fraction of shipped parts that are defective

Defect Level, Yield & Fault Coverage

$$DL \approx 1 - Y(1-T)$$

DL: defect level


Y: yield

T: fault coverage




Yield (Y)	Fault Coverage (T)	DPM (DL)
50%	90%	67,000
75%	90%	28,000
90%	90%	10,000
95%	90%	5,000
99%	90%	1,000
90%	90%	10,000
90%	95%	5,000
90%	99%	1,000
90%	99.9%	100

Single Stuck-at Fault

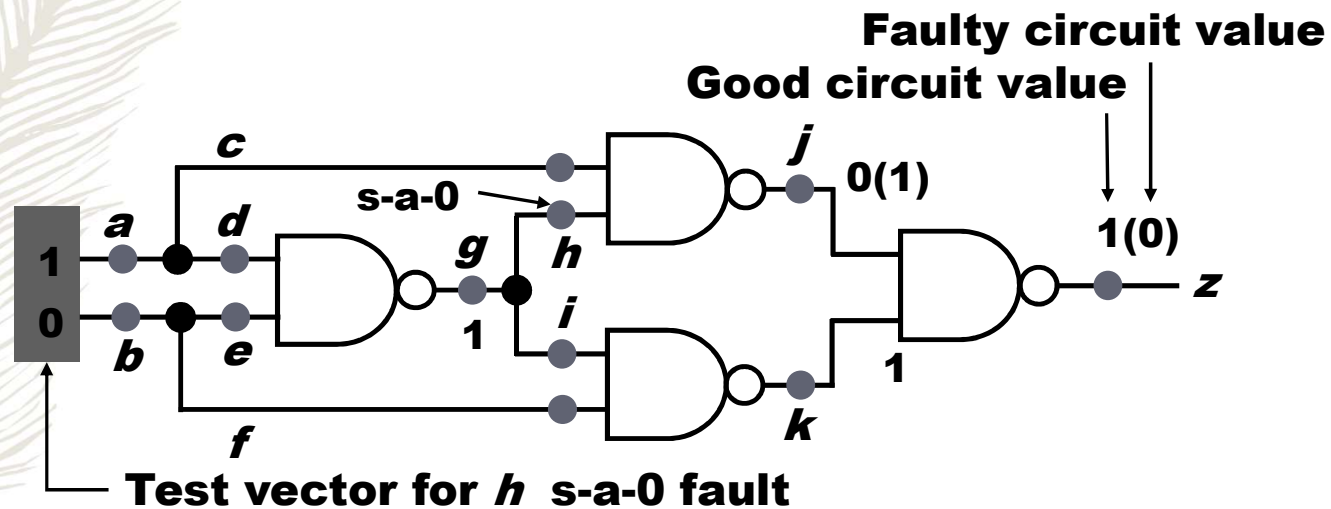- Three properties define a single stuck-at fault
 - Only one line is faulty
 - The faulty line is permanently set to 0 or 1
 - The fault can be at an input or output of a gate
- Example: XOR circuit has 12 fault sites (●) and 24 single stuck-at faults



Examples

   

Design Strategies for Test:

- Observability: ease of observing a node by watching external output pins of the chip
- Controllability: ease of forcing a node to 0 or 1 by driving input pins of the chip
- Combinational logic is usually easy to observe and control
- Finite state machines can be very difficult, requiring many cycles to enter desired state
 - Especially if state transition diagram is not known to the test engineer


Test Pattern Generation

- Manufacturing test ideally would check every node in the circuit to prove it is not stuck.
- Apply the smallest sequence of test vectors necessary to prove each node is not stuck.
- Good observability and controllability reduces number of test vectors required for manufacturing test.
 - Reduces the cost of testing
 - Motivates design-for-test

Test Example


	SA1	SA0
➤ A3	{0110}	{1110}
➤ A2	{1010}	{1110}
➤ A1	{0100}	{0110}
➤ A0	{0110}	{0111}
➤ n1	{11	{0110}
➤ n2	{0110}	{0100}
➤ n3	{0101}	{0110}
➤ Y	{0110}	{1110}

 - Minimum set: {0100, 0101, 0110, 0111, 1010, 1110}




Design for Test

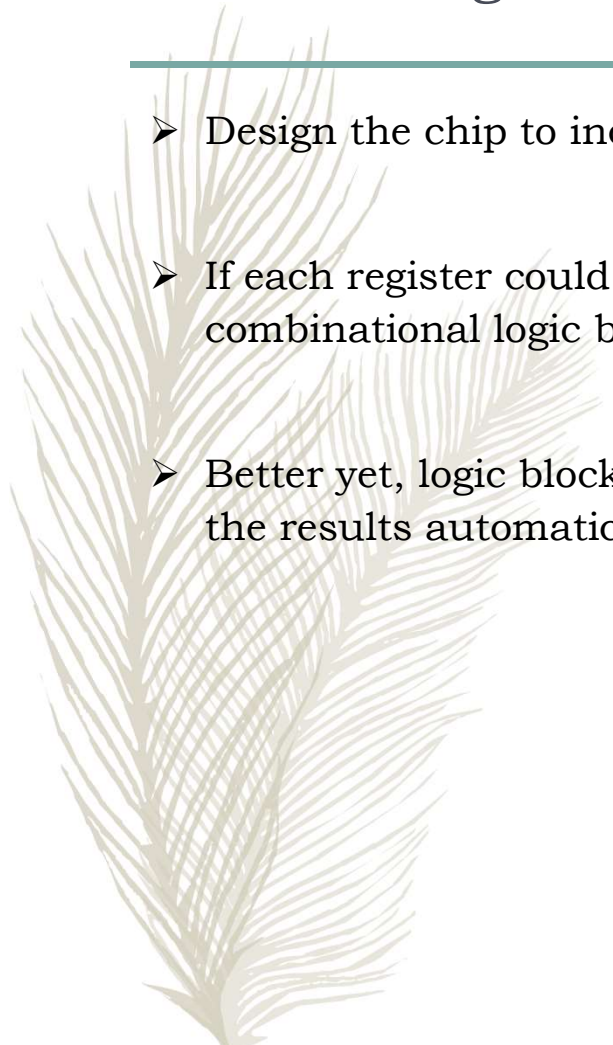- Design the chip to increase observability and controllability
- If each register could be observed and controlled, test problem reduces to testing combinational logic between registers.
- Better yet, logic blocks could enter test mode where they generate test patterns and report the results automatically.




Scan




 
- Convert each flip-flop to a scan register
 - Only costs one extra multiplexer
 - Normal mode: flip-flops behave as usual
 - Scan mode: flip-flops behave as shift register



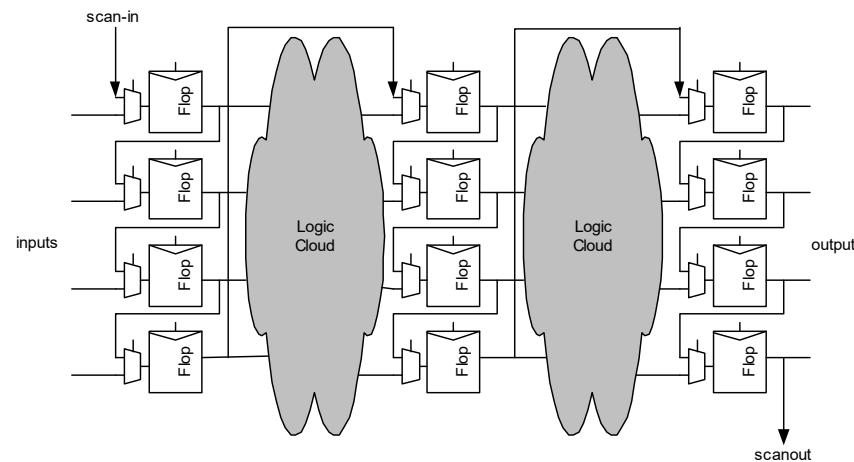- Contents of flops
 - can be scanned out and new values scanned in



Scannable Flip-flops

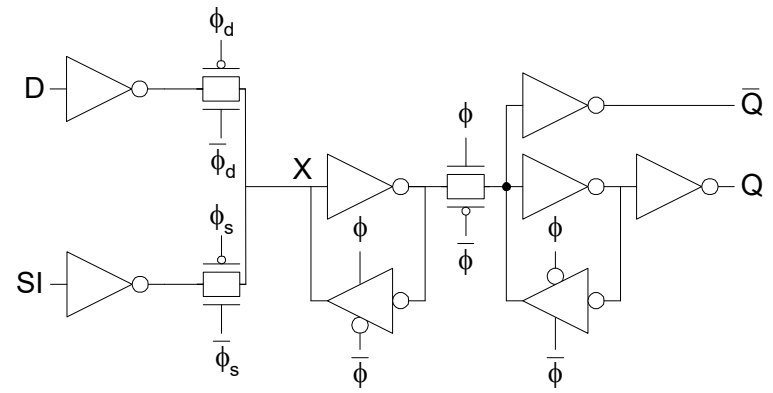 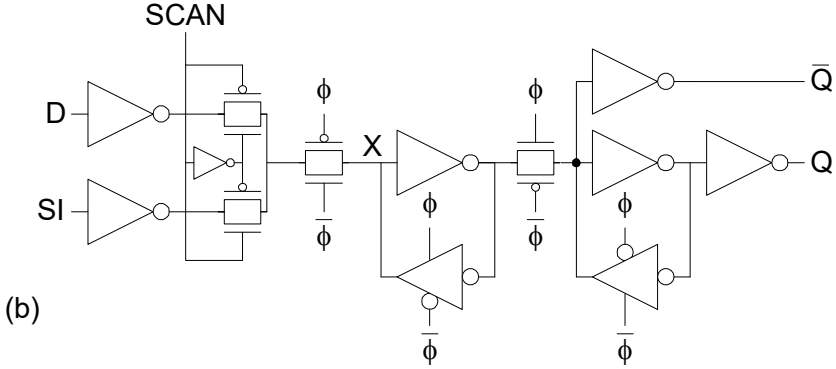 


ATPG

- Test pattern generation is tedious
- Automatic Test Pattern Generation (ATPG) tools produce a good set of vectors for each block of combinational logic
- Scan chains are used to control and observe the blocks
- Complete coverage requires a large number of vectors, raising the cost of test
- Most products settle for covering 90+% of potential stuck-at faults




Built-in Self-test

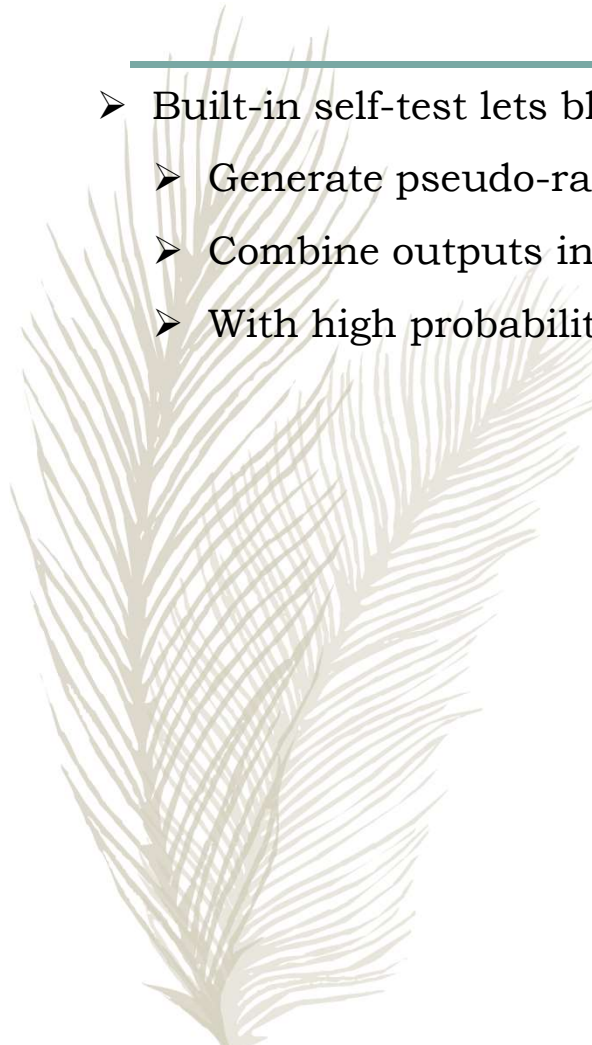- Built-in self-test lets blocks test themselves
 - Generate pseudo-random inputs to comb. logic
 - Combine outputs into a syndrome
 - With high probability, block is fault-free if it produces the expected syndrome




General Architecture of BIST

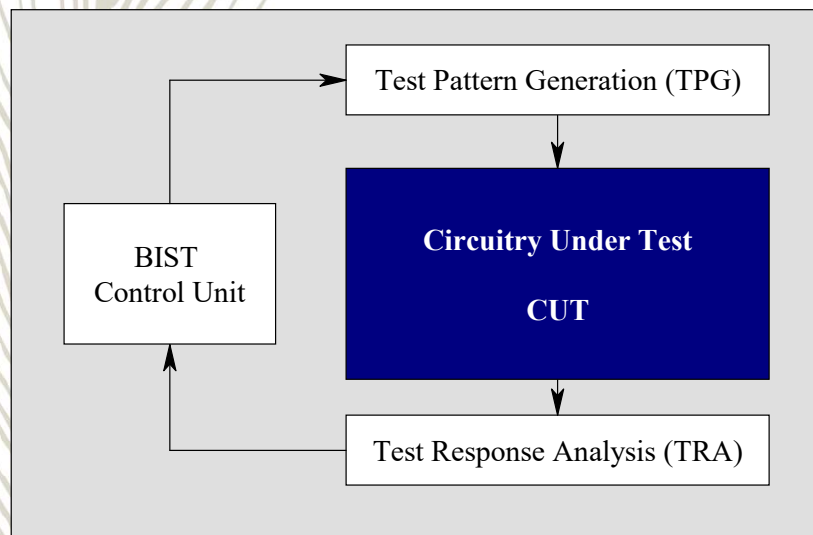

- BIST components:
 - Test pattern generator (TPG)
 - Test response analyzer (TRA)
- TPG & TRA are usually implemented as linear feedback shift registers (LFSR)
- Two widespread schemes:
 - test-per-scan
 - test-per-clock

Pattern Generation


Pseudorandom Test generation by LFSR:

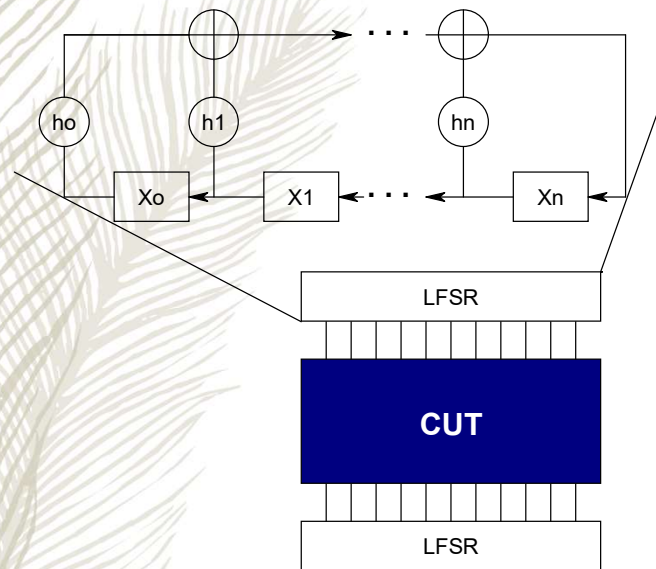

- Using special LFSR registers
- Several proposals:
 - BILBO
 - CSTP
- Main characteristics of LFSR:
 - polynomial
 - initial state
 - test length

PRSG

 
- Linear Feedback Shift Register
 - Shift register with input taken from XOR of state
 - Pseudo-Random Sequence Generator



Step	Y
0	111
1	110
2	101
3	010
4	100
5	001
6	011
7	111 (repeats)


BILBO

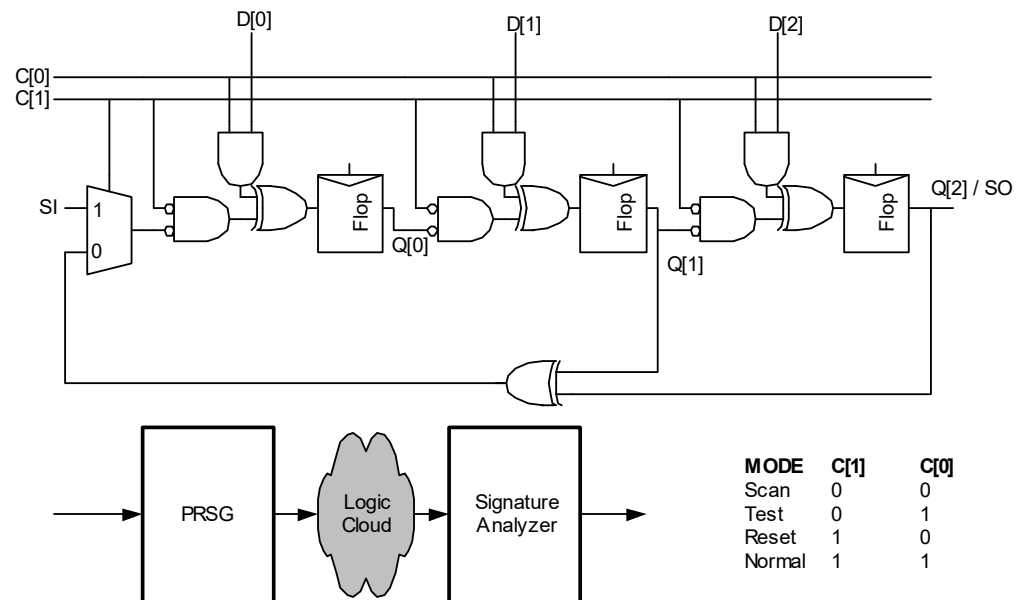- Built-in Logic Block Observer
- Combine scan with PRSG & signature analysis




Boundary Scan

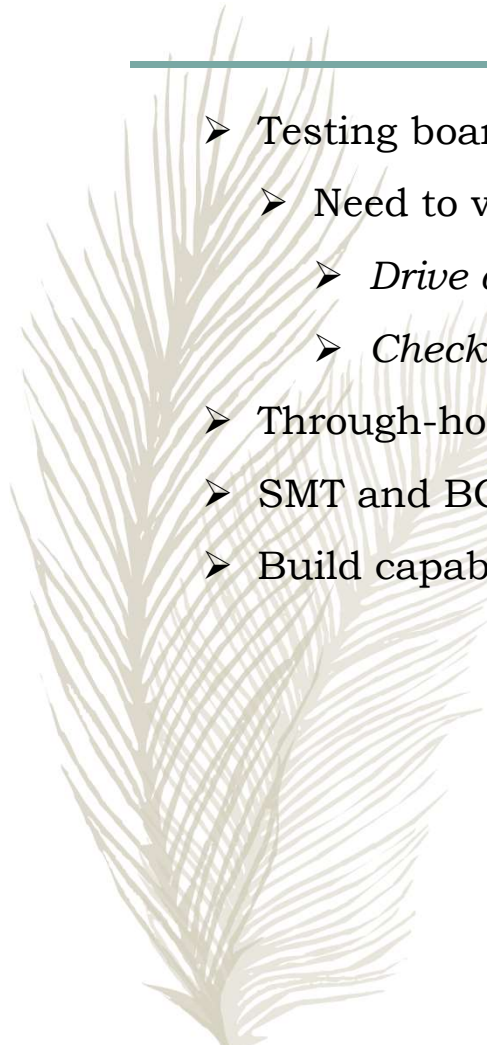- Testing boards is also difficult
 - Need to verify solder joints are good
 - *Drive a pin to 0, then to 1*
 - *Check that all connected pins get the values*
 - Through-hole boards used “bed of nails”
 - SMT and BGA boards cannot easily contact pins
 - Build capability of observing and controlling pins into each chip to make board test easier




Boundary Scan Example

 

Boundary Scan Interface

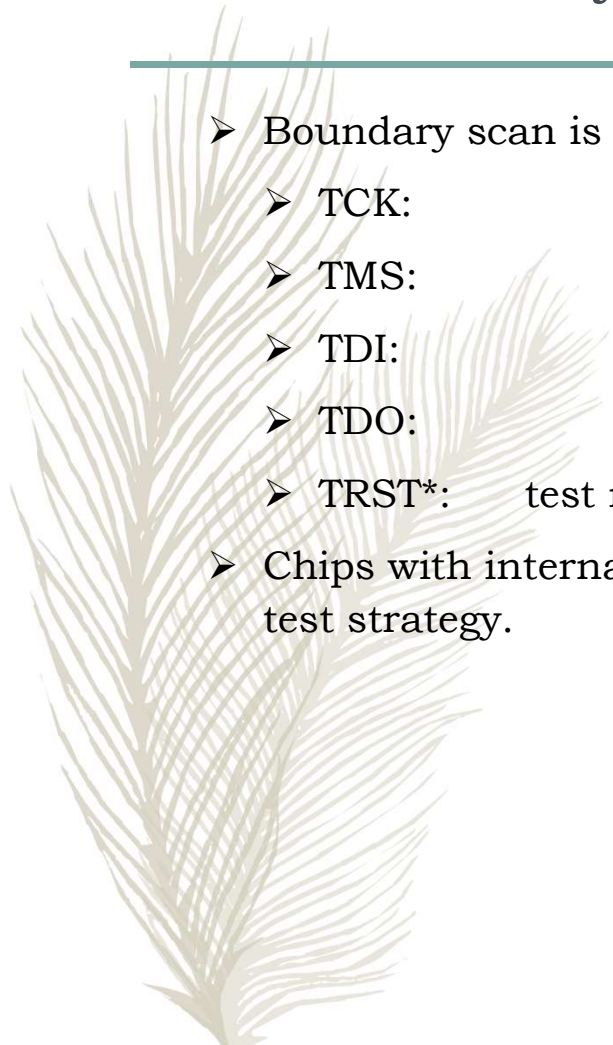- Boundary scan is accessed through five pins
 - TCK: test clock
 - TMS: test mode select
 - TDI: test data in
 - TDO: test data out
 - TRST*: test reset (optional)
- Chips with internal scan chains can access the chains through boundary scan for unified test strategy.



Some Definitions

- **LFSR** – Linear feedback shift register, hardware that generates pseudo-random pattern sequence
- **BILBO** – Built-in logic block observer, extra hardware added to flip-flops so they can be reconfigured as an LFSR pattern generator or response compacter, a scan chain, or as flip-flops
- **Exhaustive testing** – Apply all possible 2^n patterns to a circuit with n inputs
- **Pseudo-exhaustive testing** – Break circuit into small, overlapping blocks and test each exhaustively
- **Pseudo-random testing** – Algorithmic pattern generator that produces a subset of all possible tests with most of the properties of randomly-generated patterns



Thank you.....

Department of Electronics and Communication Engineering, VBIT

VIDYA SAGAR P